

Topics:

- Modes of 555 Timer IC
- Waveform Generation using Astable Multivibrator


- Multivibrator (555 Timer)
- Modes of Multivibrator (555 Timer)
 - Waveform Representation of Astable Multivibrator (555 Timer)
 - Waveform Representation of Monostable Multivibrator (555 Timer)
 - Waveform Representation of Bistable Multivibrator (555 Timer)
- Waveform Generation of Astable Multivibrator (555 Timer)

- Multivibrator (555 Timer)
- Modes of Multivibrator (555 Timer)
 - Waveform Representation of Astable Multivibrator (555 Timer)
 - Waveform Representation of Monostable Multivibrator (555 Timer)
 - Waveform Representation of Bistable Multivibrator (555 Timer)
- Waveform Generation of Astable Multivibrator (555 Timer)


Multivibrator (555 Timer)

Multivibrator

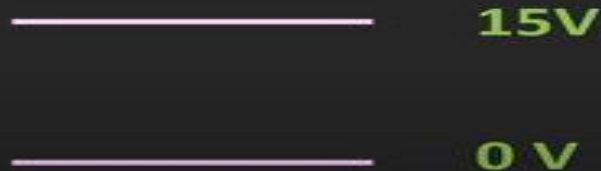
The Multivibrator is the electronic circuit which is used to implement two state devices like oscillator, timer, and Flip-Flop



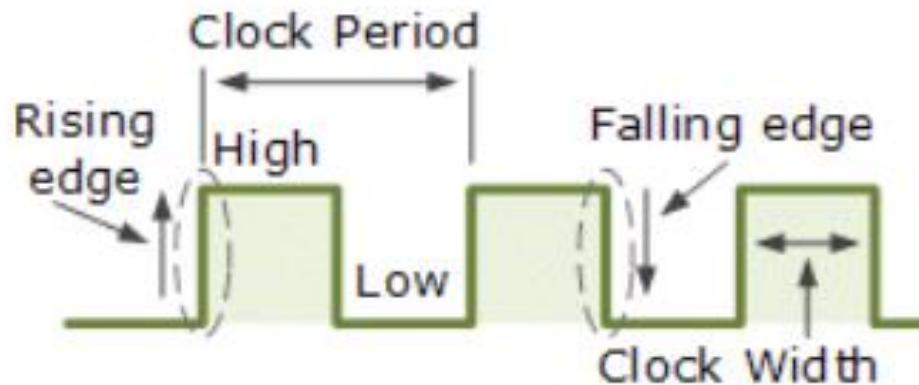- ✓ A multivibrator circuit oscillates between a “HIGH” state and a “LOW” state producing a continuous output



Multivibrator (555 Timer)

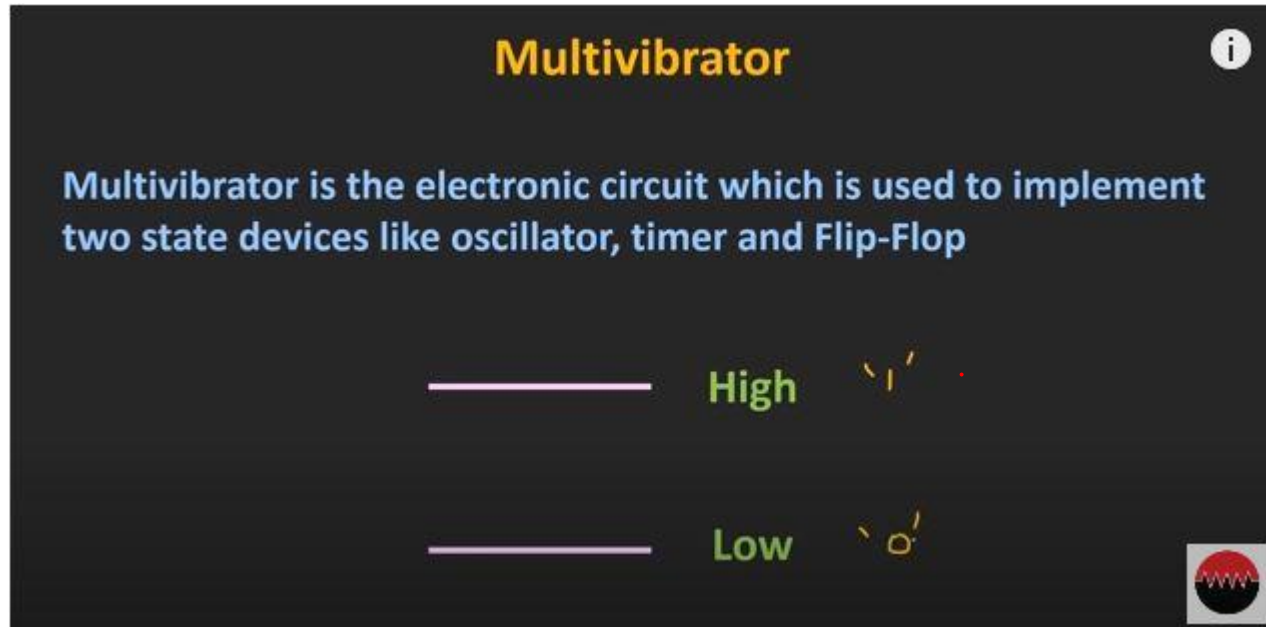

- ✓ Multivibrators produce an output wave shape resembling that of a symmetrical or asymmetrical square wave
- ✓ Multivibrators have two different electrical states, an output “HIGH” state and an output “LOW” state giving them either a stable or quasi-stable state depending upon the type of multivibrator


- Multivibrator (555 Timer)
- Modes of Multivibrator (555 Timer)
 - Waveform Representation of Astable Multivibrator (555 Timer)
 - Waveform Representation of Monostable Multivibrator (555 Timer)
 - Waveform Representation of Bistable Multivibrator (555 Timer)
- Waveform Generation of Astable Multivibrator (555 Timer)

Modes of Multivibrator (555 Timer)

- ✓ Astable Multivibrator
- ✓ **Monostable Multivibrator**
- ✓ Bistable Multivibrator

- Multivibrator (555 Timer)
- Modes of Multivibrator (555 Timer)
 - Waveform Representation of Astable Multivibrator (555 Timer)
 - Waveform Representation of Monostable Multivibrator (555 Timer)
 - Waveform Representation of Bistable Multivibrator (555 Timer)
- Waveform Generation of Astable Multivibrator (555 Timer)

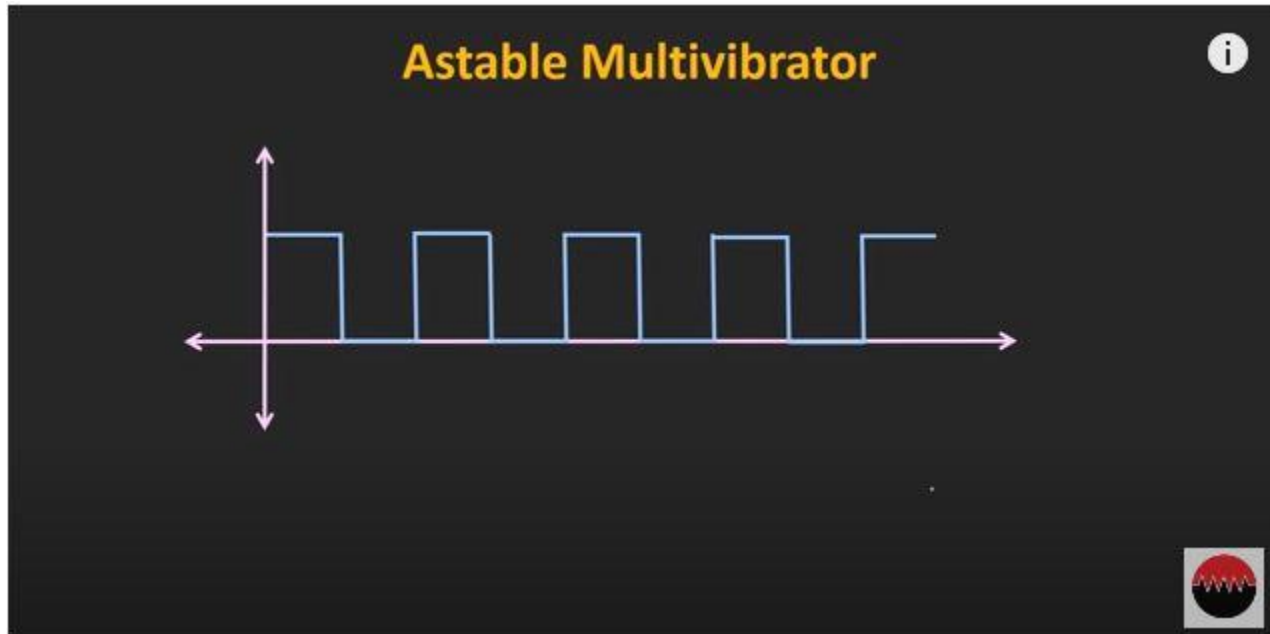Waveform Representation of Astable Multivibrator (555 Timer)




- ✓ Astable: A free-running multivibrator that has **NO** stable states but switches continuously between two states this action produces a train of square wave pulses at a fixed known frequency

Astable Multivibrator (555 Timer)


- ✓ These circuits are not stable in any state and switch outputs after predetermined time periods
- ✓ The result of this is that the output is a continuous square/rectangular wave with the properties depending on values of external resistors and capacitors
- ✓ Thus, while designing these circuits following parameters need to be determined:
 1. Frequency (or the time period) of the wave
 2. The duty cycle of the wave

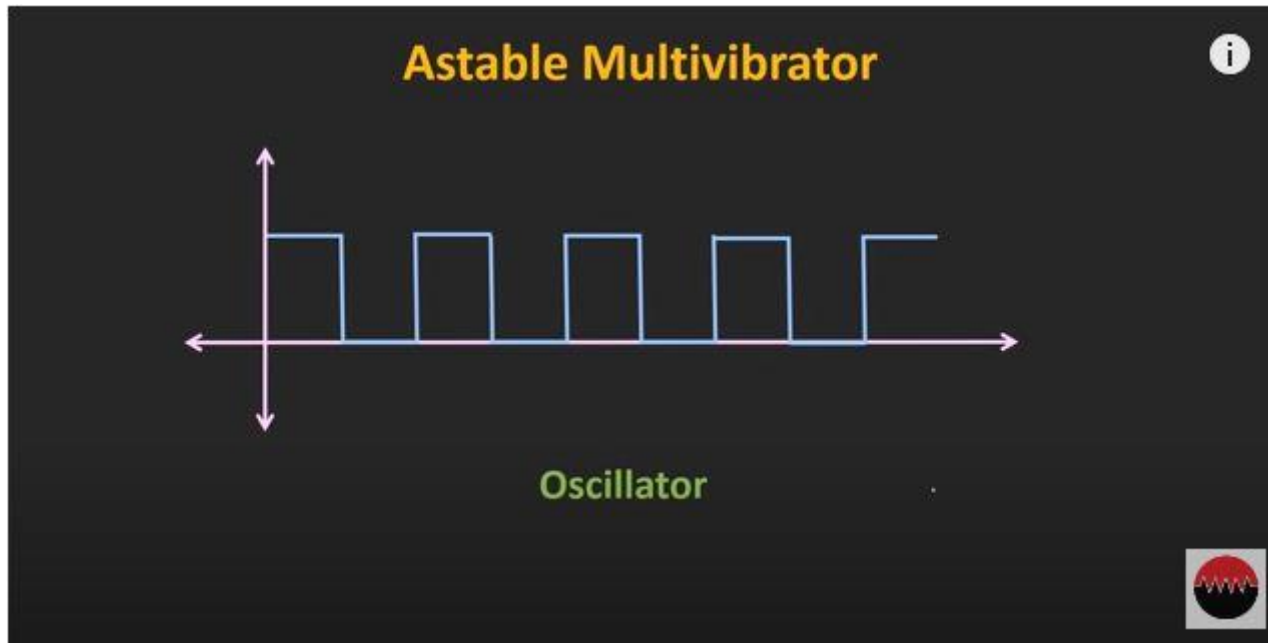Waveform Representation of Astable Multivibrator (555 Timer)




- Multivibrator (555 Timer)
- Modes of Multivibrator (555 Timer)
 - Waveform Representation of Astable Multivibrator (555 Timer)
 - Waveform Representation of Monostable Multivibrator (555 Timer)
 - Waveform Representation of Bistable Multivibrator (555 Timer)
- Waveform Generation of Astable Multivibrator (555 Timer)

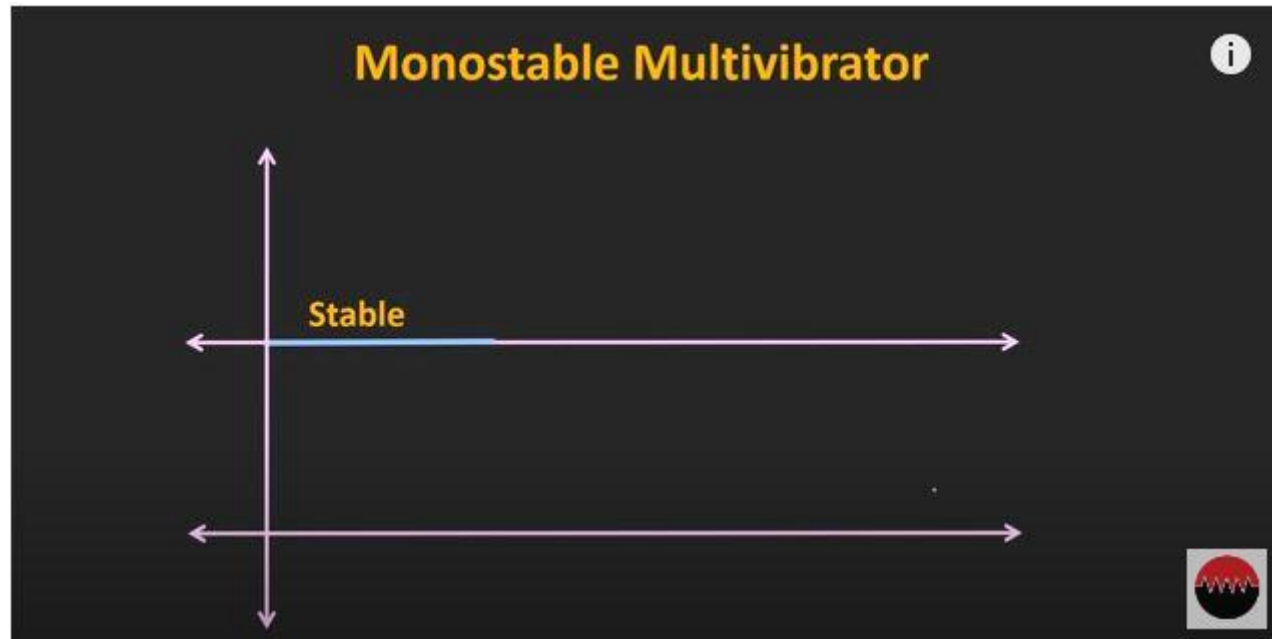Waveform Representation of Monostable Multivibrator (555 Timer)




- ✓ **Monostable Multivibrators** have only **ONE** stable state (hence their name: “Mono”), and produce a single output pulse when it is triggered externally

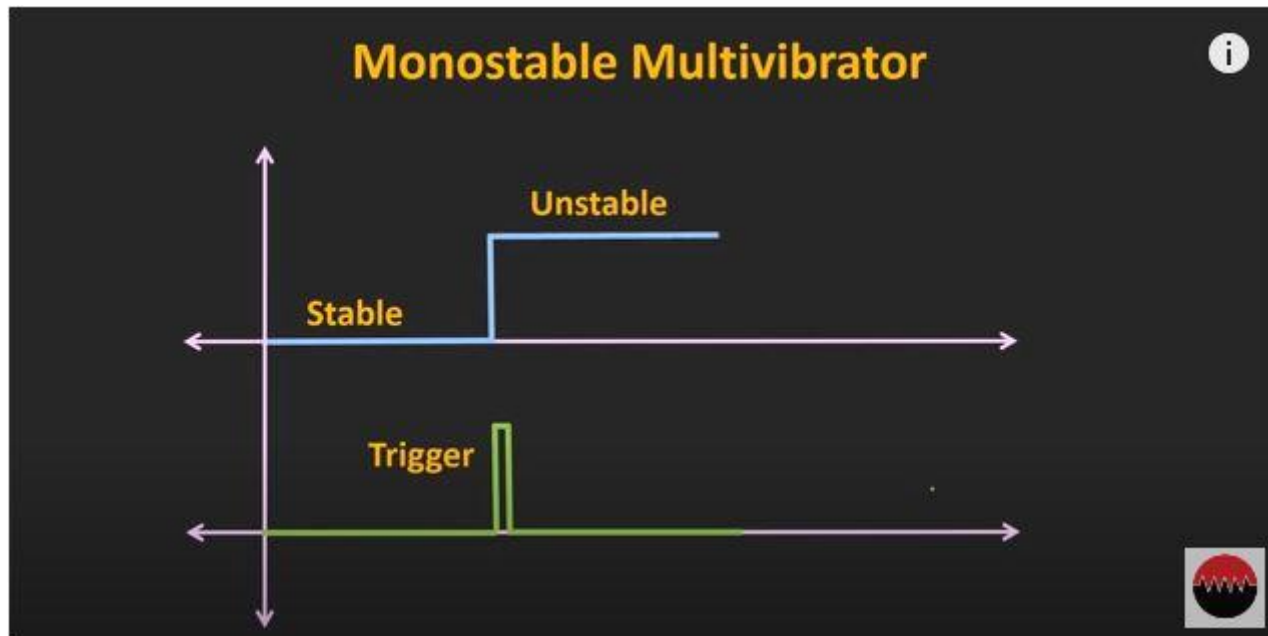
Waveform Representation of Monostable Multivibrator (555 Timer)



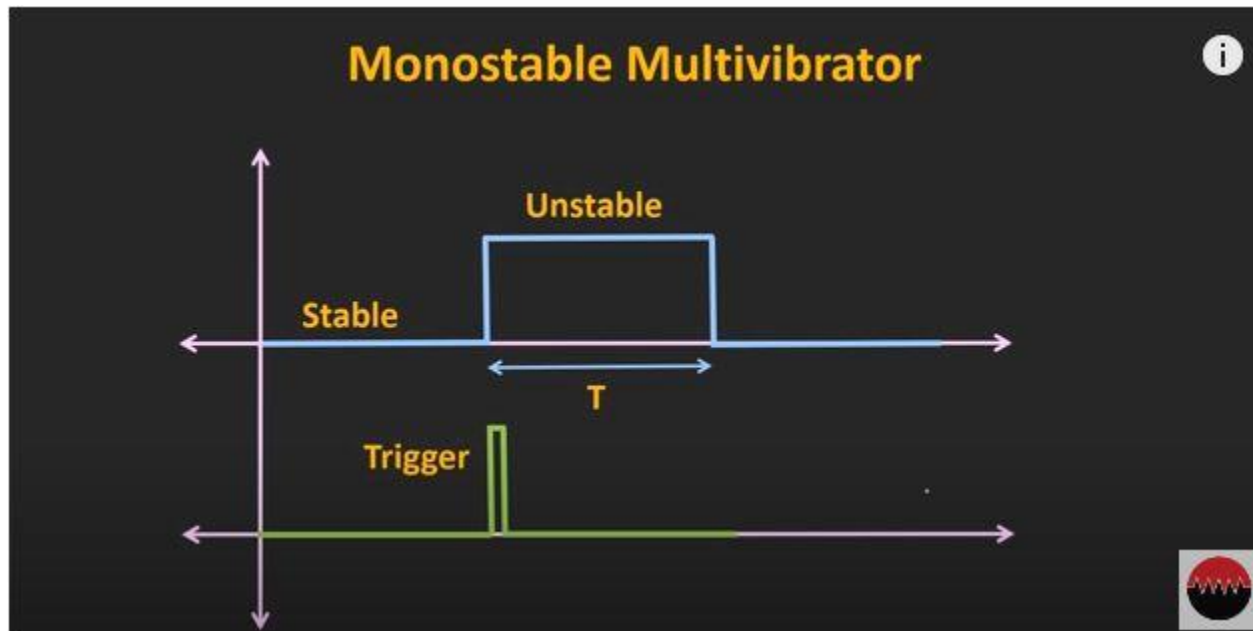
Waveform Representation of Monostable Multivibrator (555 Timer)



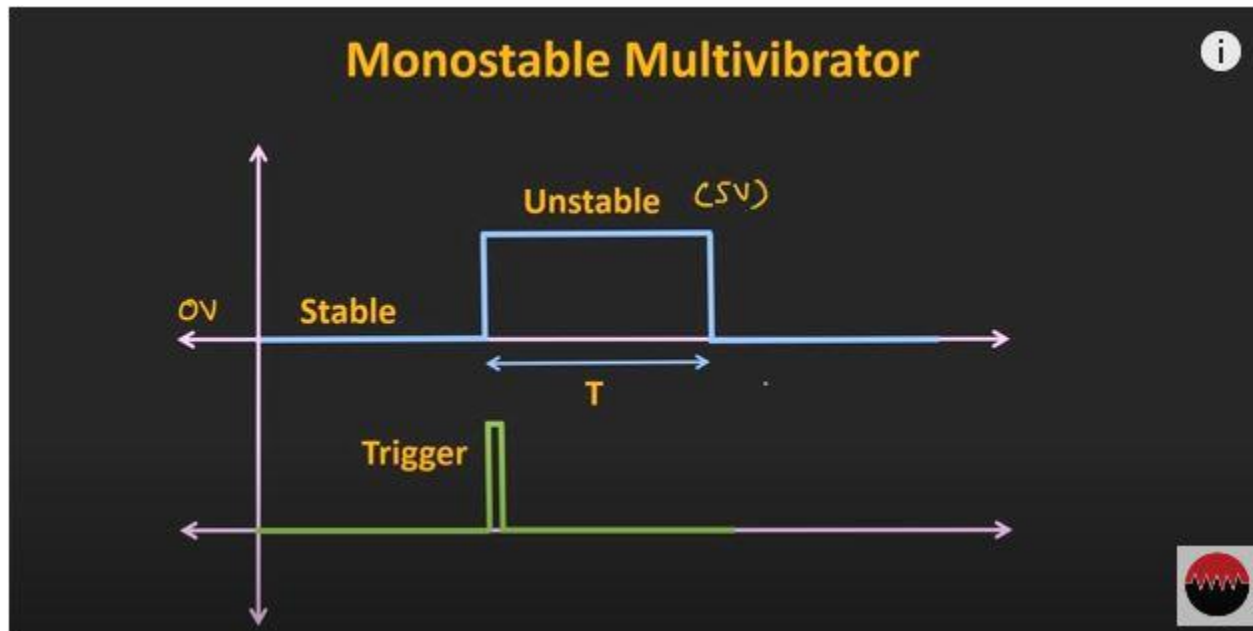
Waveform Representation of Monostable Multivibrator (555 Timer)



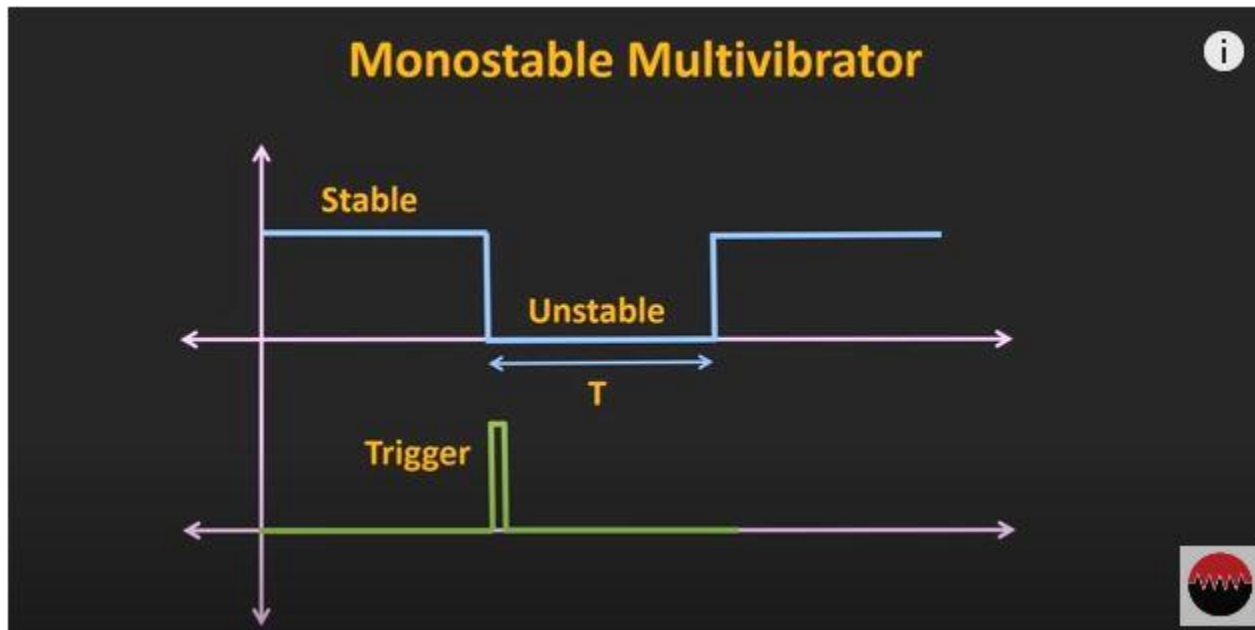
Waveform Representation of Monostable Multivibrator (555 Timer)



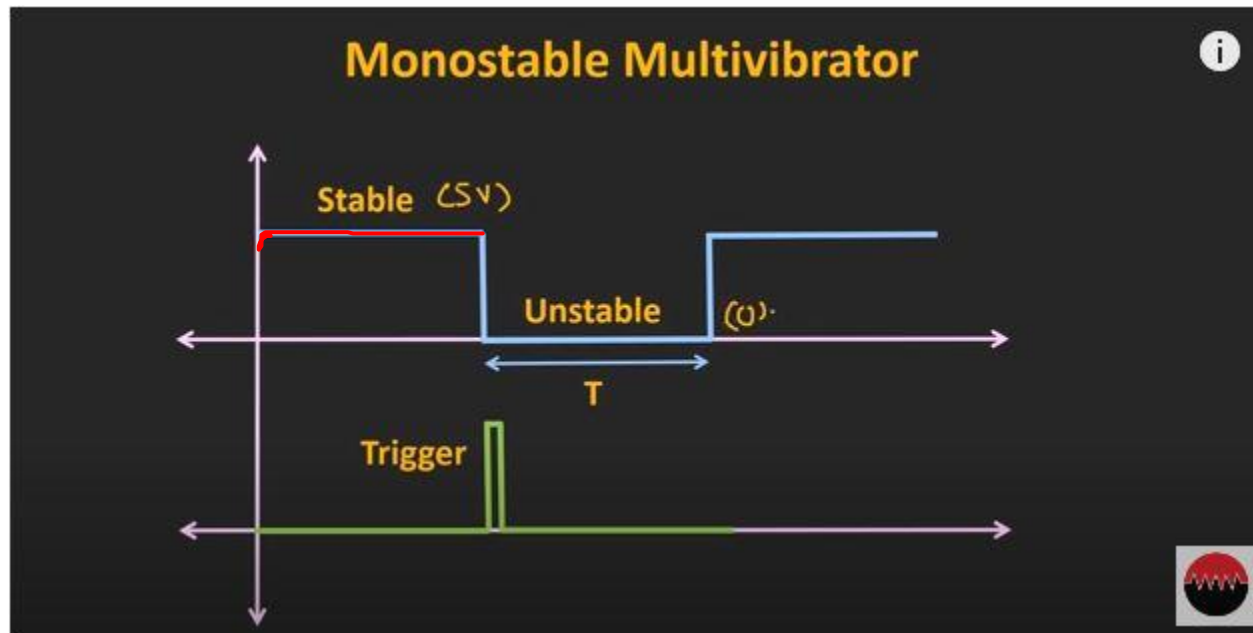Waveform Representation of Monostable Multivibrator (555 Timer)




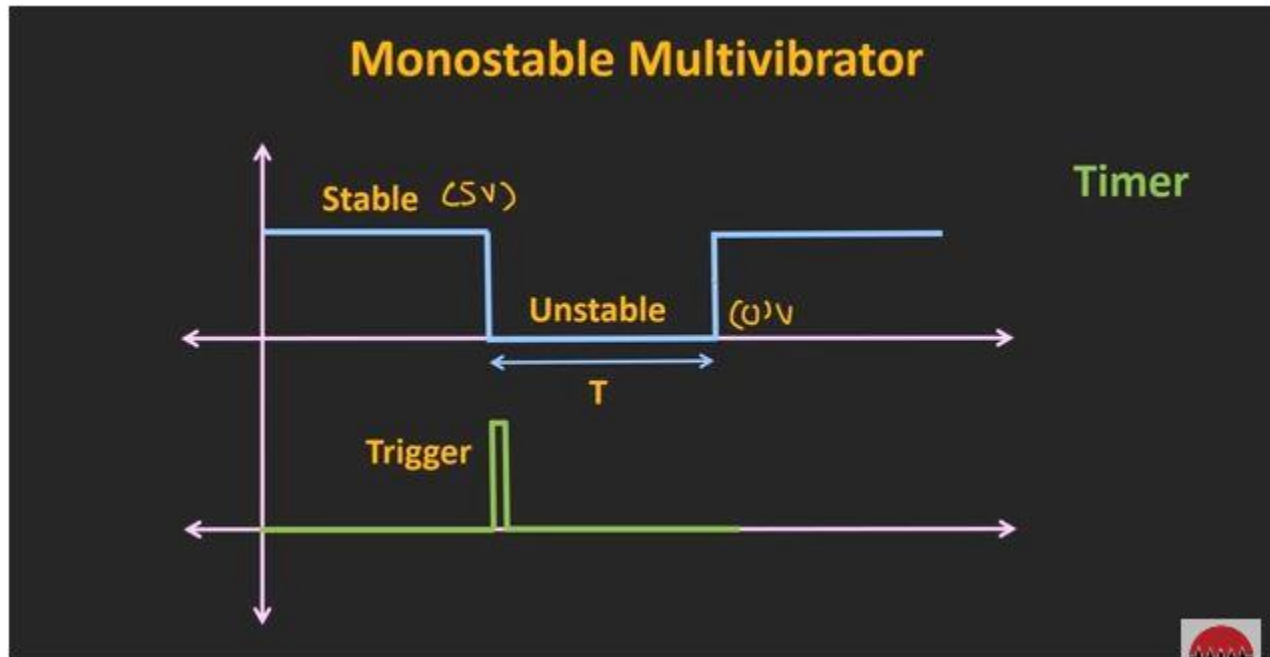Waveform Representation of Monostable Multivibrator (555 Timer)




- Multivibrator (555 Timer)
- Modes of Multivibrator (555 Timer)
 - Waveform Representation of Astable Multivibrator (555 Timer)
 - Waveform Representation of Monostable Multivibrator (555 Timer)
 - Waveform Representation of Bistable Multivibrator (555 Timer)
- Waveform Generation of Astable Multivibrator (555 Timer)

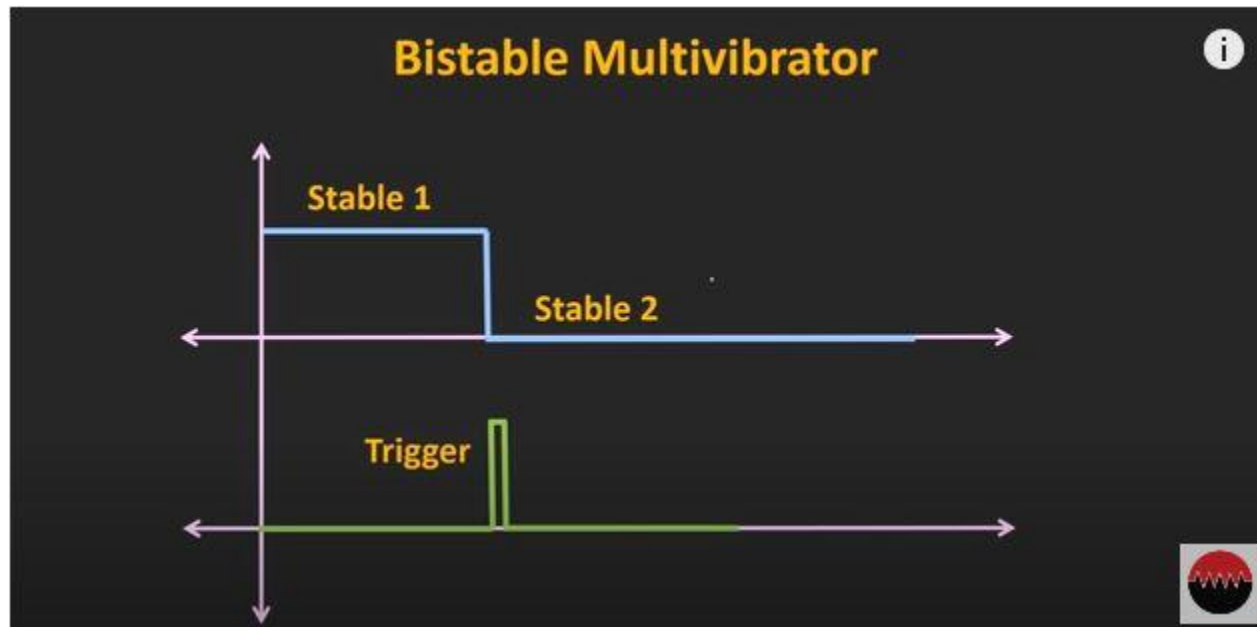Waveform Representation of Bistable Multivibrator (555 Timer)




- ✓ The **Bistable Multivibrator** is another type of two state device similar to the Monostable Multivibrator
- ✓ BOTH states are stable



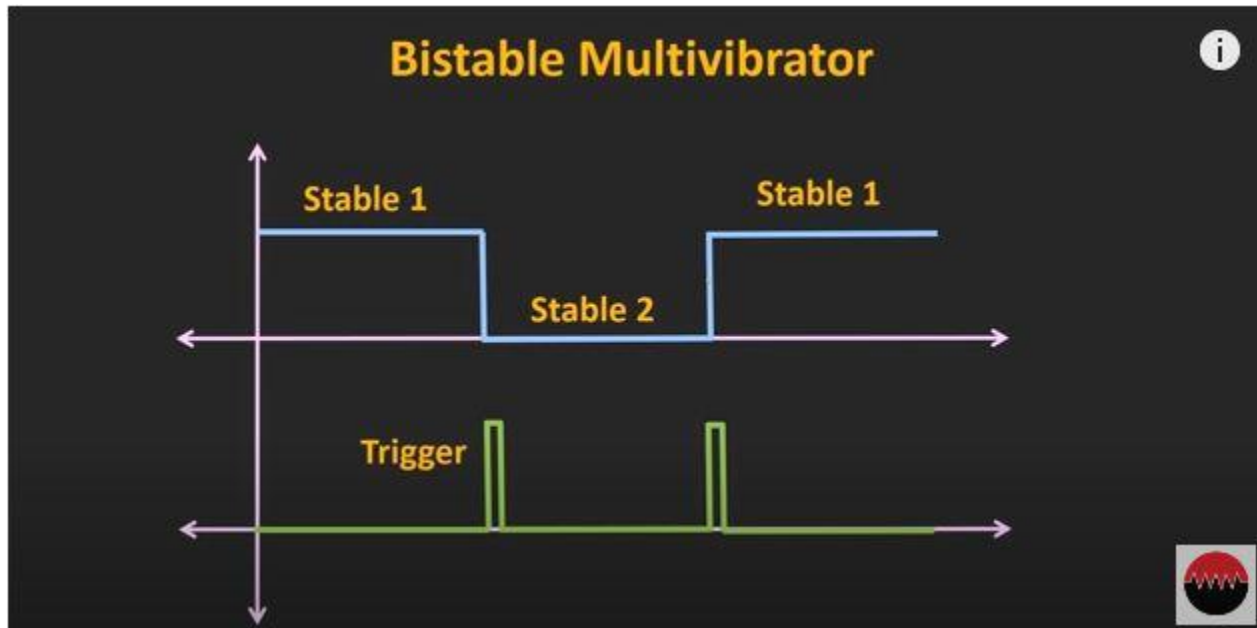
Waveform Representation of Bistable Multivibrator (555 Timer)



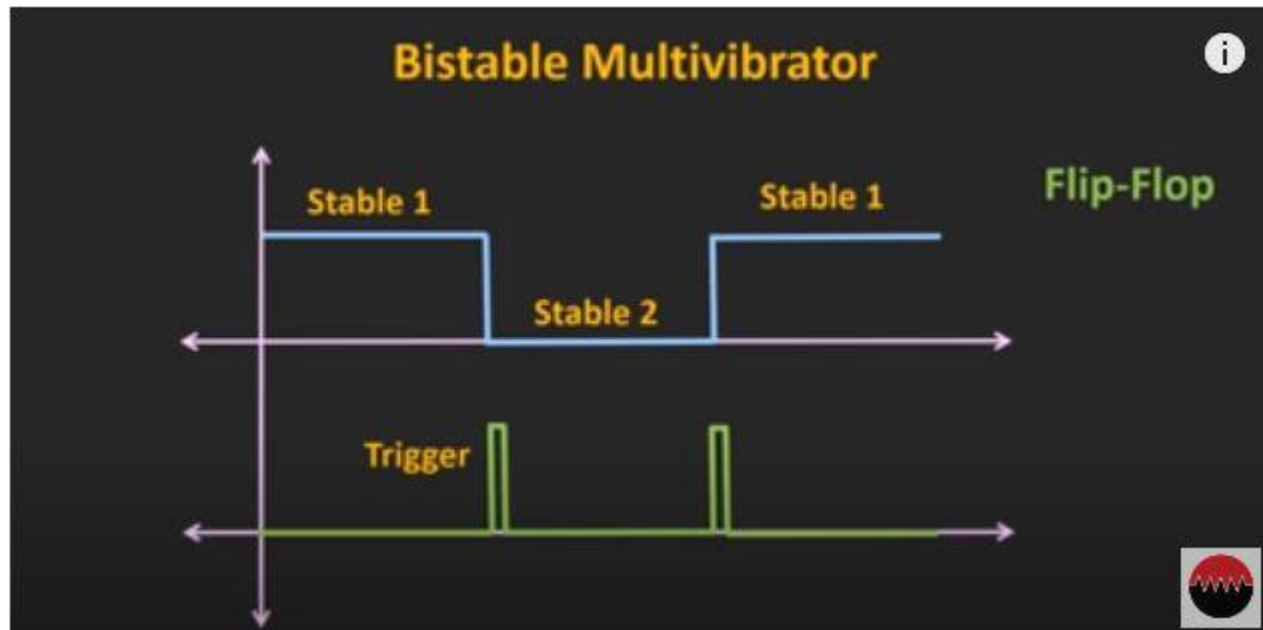Waveform Representation of Bistable Multivibrator (555 Timer)




Pin Diagram of 555 Timer

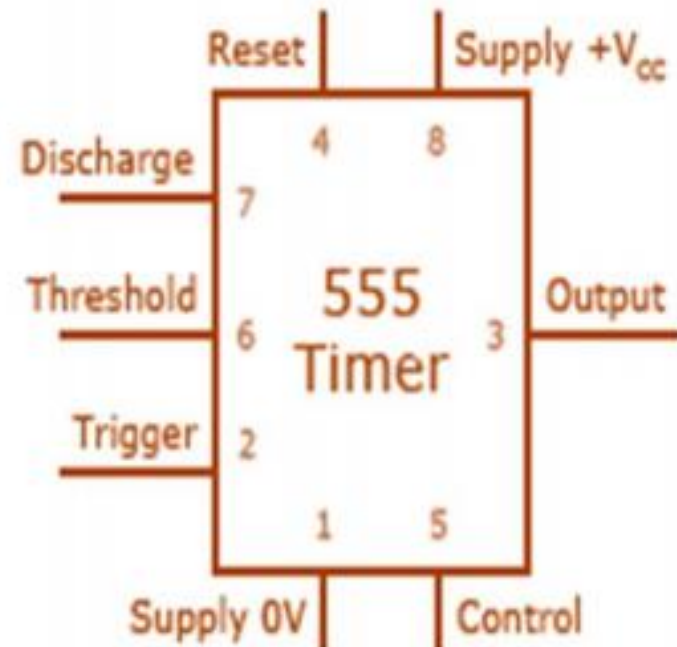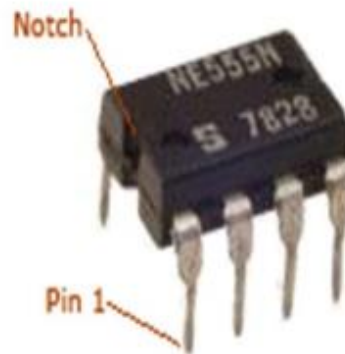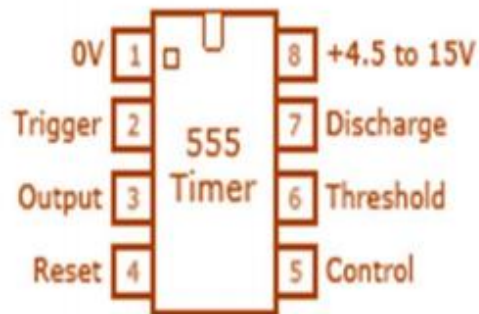

Pin Configuration

- Pin 1. – **Ground**, The ground pin connects the 555 timer to the negative (0v) supply rail.
- Pin 2. – **Trigger**, The negative input to comparator No 1. A negative pulse on this pin “sets” the internal Flip-flop when the voltage drops below $1/3V_{cc}$ causing the output to switch from a “LOW” to a “HIGH” state.
- Pin 3. – **Output**, The output pin can drive any TTL circuit and is capable of sourcing or sinking up to 200mA of current at an output voltage equal to approximately $V_{cc} - 1.5V$ so small speakers, LEDs or motors can be connected directly to the output.
- Pin 4. – **Reset**, This pin is used to “reset” the internal Flip-flop controlling the state of the output, pin 3. This is an active-low input and is generally connected to a logic “1” level when not used to prevent any unwanted resetting of the output.
- Pin 5. – **Control Voltage**, This pin controls the timing of the 555 by overriding the $2/3V_{cc}$ level of the voltage divider network. By applying a voltage to this pin the width of the output signal can be varied independently of the RC timing network. When not used it is connected to ground via a 10nF capacitor to eliminate any noise.
- Pin 6. – **Threshold**, The positive input to comparator No 2. This pin is used to reset the Flip-flop when the voltage applied to it exceeds $2/3V_{cc}$ causing the output to switch from “HIGH” to “LOW” state. This pin connects directly to the RC timing circuit.
- Pin 7. – **Discharge**, The discharge pin is connected directly to the Collector of an internal NPN transistor which is used to “discharge” the timing capacitor to ground when the output at pin 3 switches “LOW”.
- Pin 8. – **Supply +Vcc**, This is the power supply pin and for general purpose TTL 555 timers is between 4.5V and 15V.

555 Timer IC

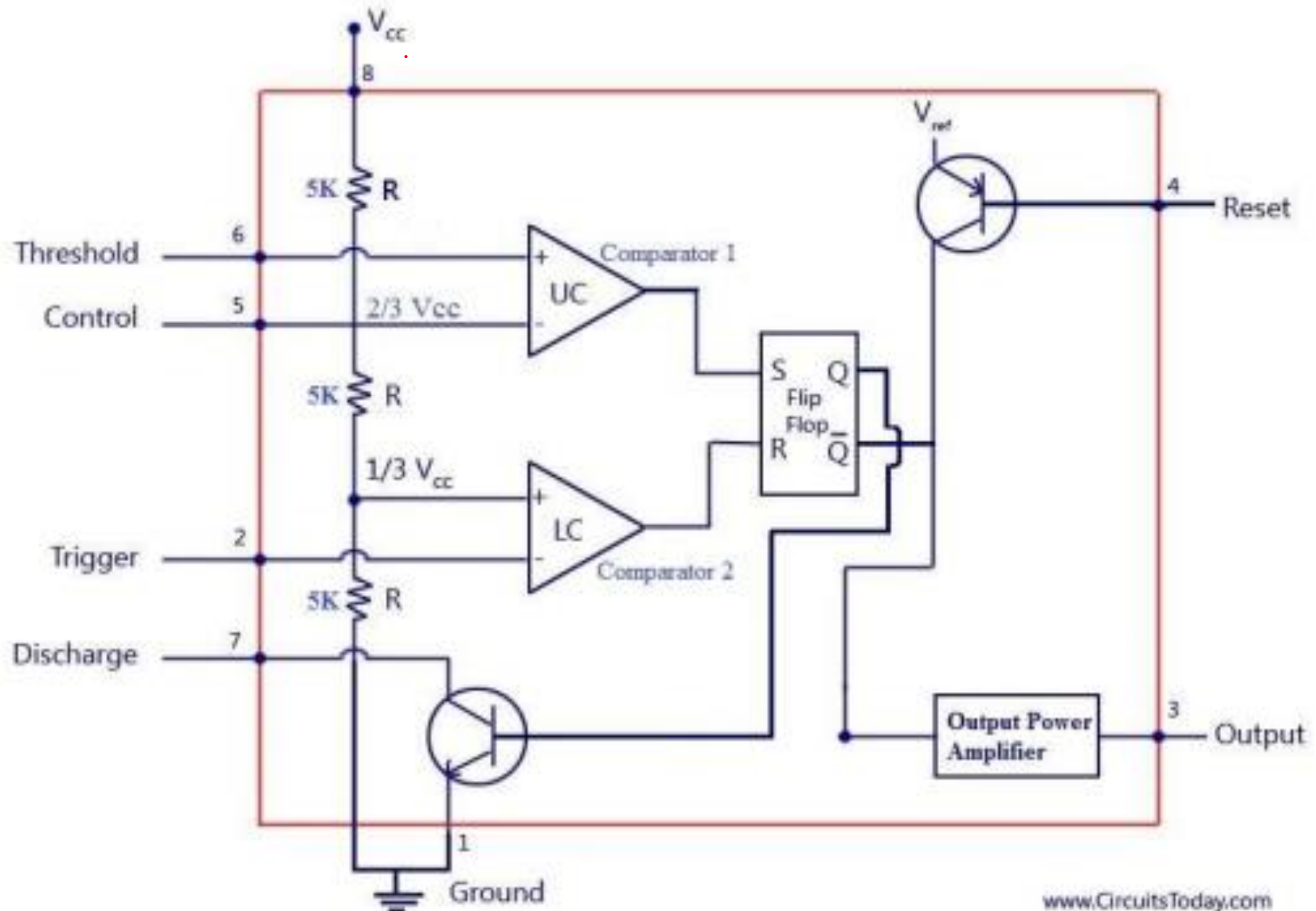


555 Timer IC (Cont...)

- ✓ A 555 timer has two comparators (which are basically Two op-amps), an R-S flip-flop, two transistors and a resistive network
- ✓ The Resistive network consists of three equal resistors (5K Ohms each R) and acts as a voltage divider
- ✓ The resistor network is designed in such a way that the voltage at the Inverting terminal of Comparator 1 (Upper comparator) will be $2/3V_{CC}$ and the voltage at the Non Inverting terminal of Comparator 2 (Lower comparator) will be $1/3V_{CC}$
- ✓ Comparator 1 – compares the threshold voltage (at pin 6) with the reference voltage + $2/3 V_{CC}$ volts
- ✓ Comparator 2 – compares the trigger voltage (at pin 2) with the reference voltage + $1/3 V_{CC}$ volts. In most applications, the control input is not used, so that the control voltage equals $+(2/3) V_{CC}$

555 Timer IC (Cont...)


- ✓ Upper comparator has a threshold input (pin 6) and a control input (pin 5)
- ✓ Output of the upper comparator is applied to set (S) input of the flip-flop
- ✓ Whenever the threshold voltage exceeds the control voltage, the upper comparator will set the flip-flop and its output is high
- ✓ A high output from the flip-flop when given to the base of the discharge transistor saturates it and thus discharges the transistor that is connected externally to the discharge pin 7
- ✓ The complementary signal out of the flip-flop goes to pin 3, the output.
- ✓ The output available at pin 3 is low
- ✓ These conditions will prevail until lower comparator triggers the flip-flop
- ✓ Even if the voltage at the threshold input falls below $(2/3) V_{CC}$ that is upper comparator cannot cause the flip-flop to change again
- ✓ To change the output of flip-flop to low, the voltage at the trigger input must fall below $+ (1/3) V_{CC}$
- ✓ When this occurs, lower comparator triggers the flip-flop, forcing its output low
- ✓ The low output from the flip-flop turns the discharge transistor off and forces the power amplifier to output a high These conditions will continue independent of the voltage on the trigger input
- ✓ Lower comparator can only cause the flip-flop to output low

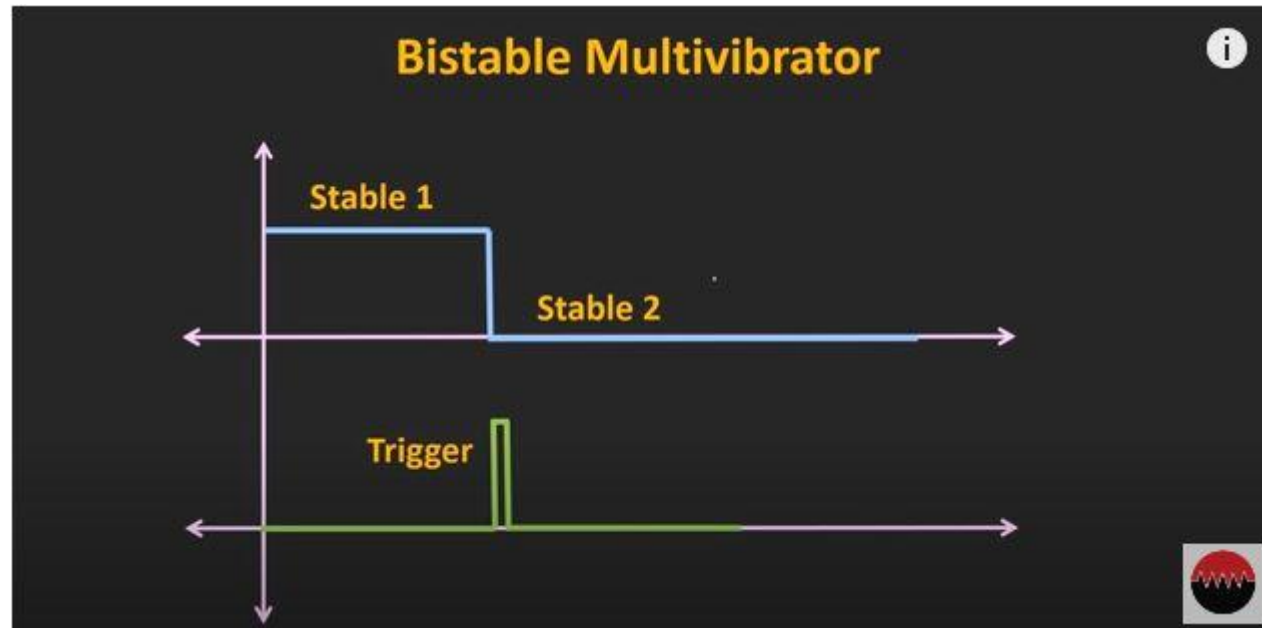Waveform Representation of Bistable Multivibrator (555 Timer)





- ✓ A flip-flop that has **TWO** stable states producing a single pulse either HIGH or LOW in value

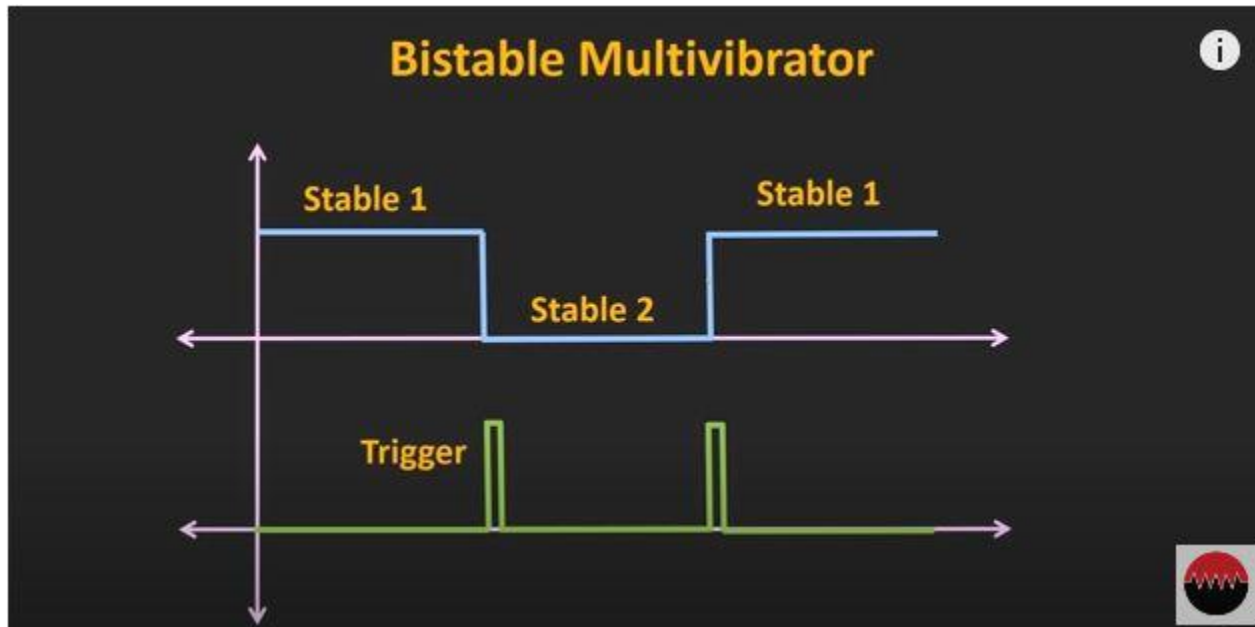Waveform Representation of Bistable Multivibrator (555 Timer)



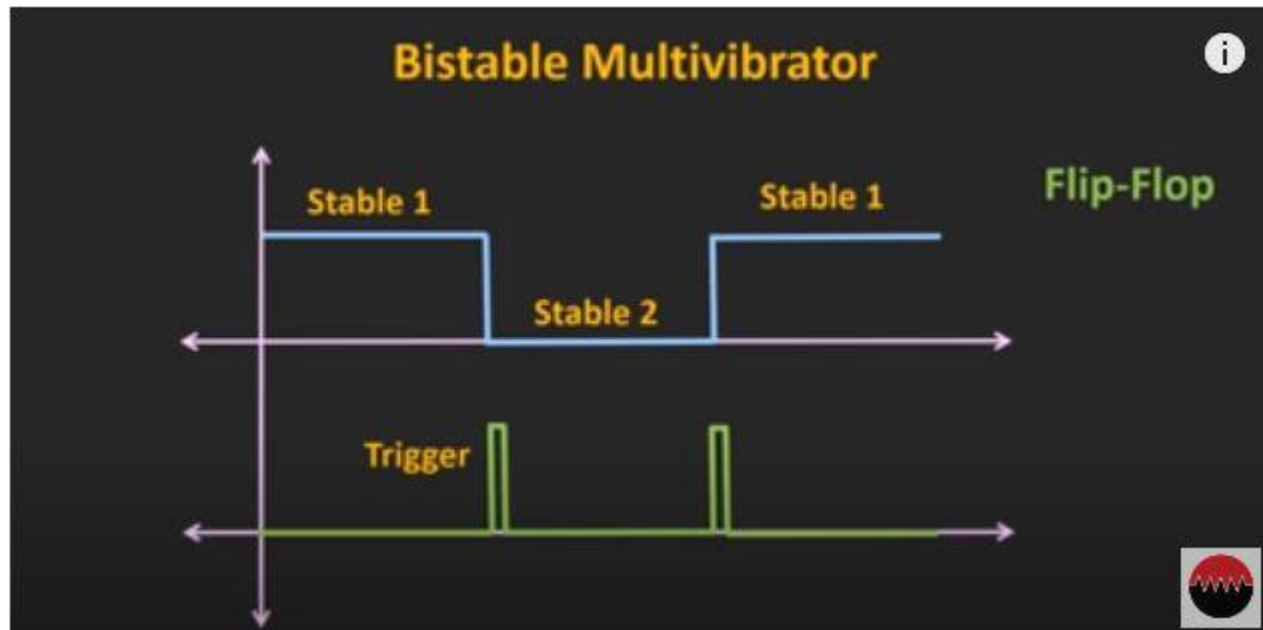Waveform Representation of Bistable Multivibrator (555 Timer)



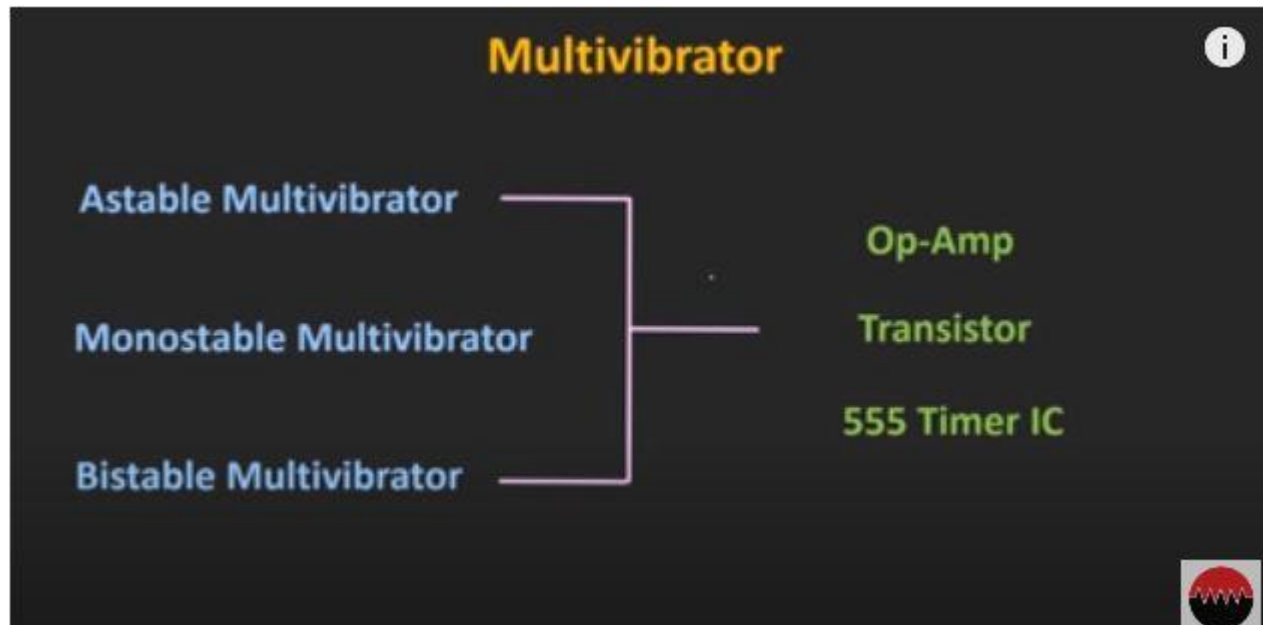

- Multivibrator (555 Timer)
- Modes of Multivibrator (555 Timer)
 - Waveform Representation of Astable Multivibrator (555 Timer)
 - Waveform Representation of Monostable Multivibrator (555 Timer)
 - Waveform Representation of Bistable Multivibrator (555 Timer)
- Waveform Generation of Astable Multivibrator (555 Timer)

Waveform Generation of Astable Multivibrator (555 Timer)




**555 Timer
as
Astable Multivibrator**

Waveform Generation of Astable Multivibrator (555 Timer)



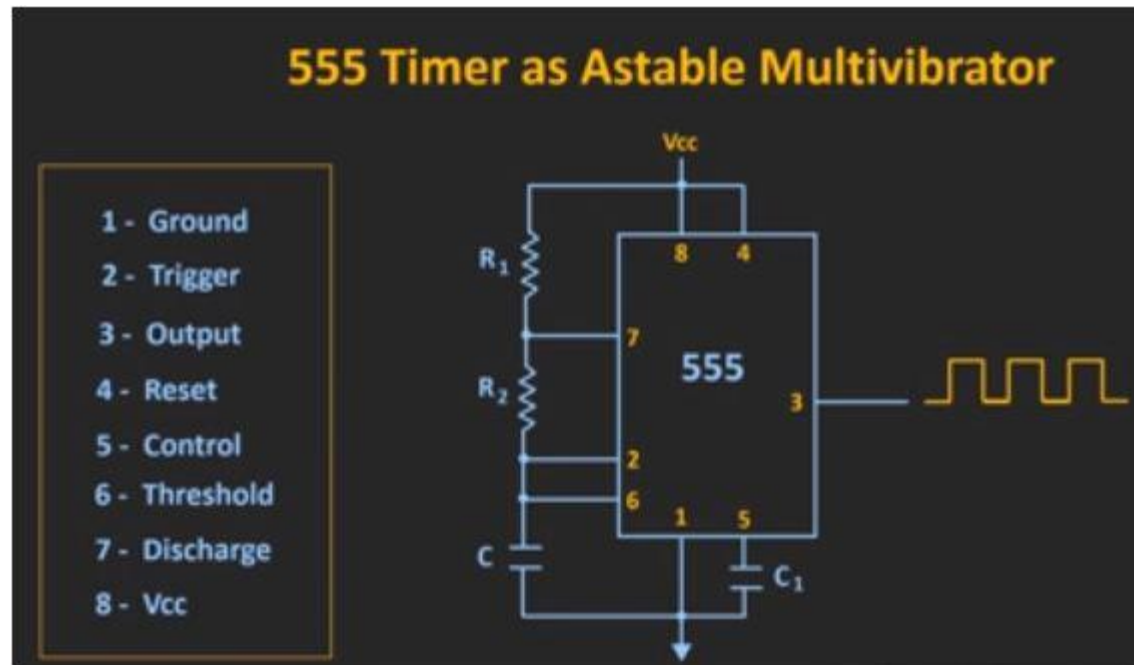Waveform Generation of Astable Multivibrator (555 Timer)




The IC 555 can be made to work as an astable multivibrator with the addition of three external components: two resistors (R_1 and R_2) and a capacitor (C)


Waveform Generation of Astable Multivibrator (555 Timer)



- ✓ An Astable Multivibrator can be designed by adding two resistors a capacitor (RA, RB and C in circuit diagram) to the 555 Timer IC
- ✓ These two resistors and the capacitor (values) are selected appropriately so as to obtain the desired 'ON' and 'OFF' timings at the output terminal (pin 3)
- ✓ So basically, the ON and OFF time at the output (i.e. the 'HIGH' and 'LOW' state at the output terminal) is dependent on the values chosen for RA, RB and C

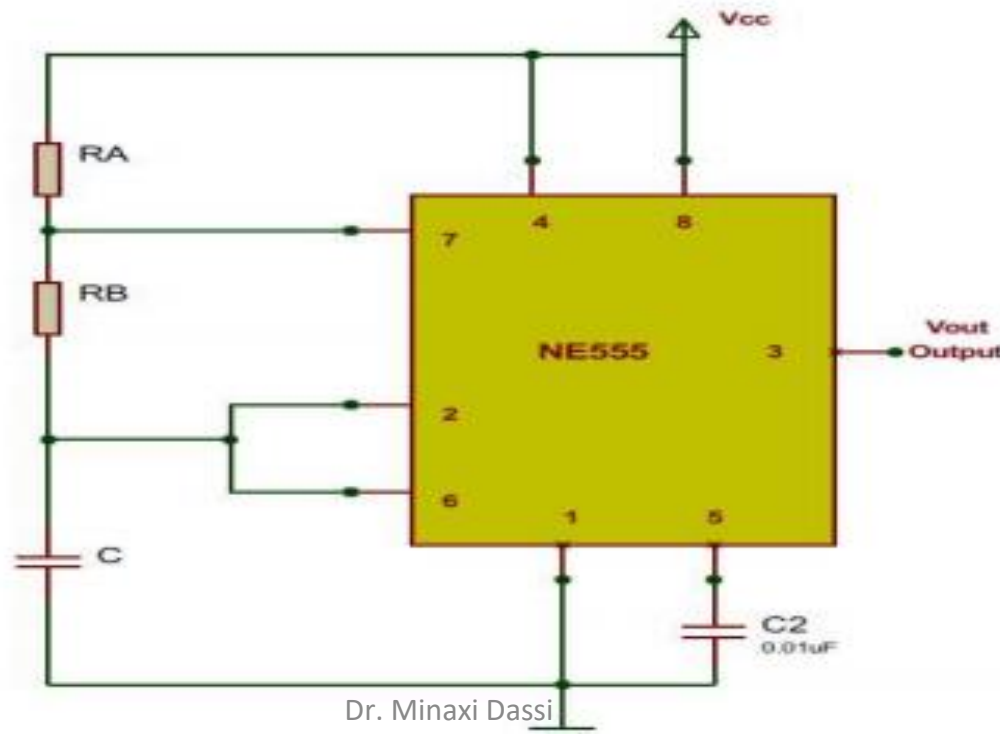


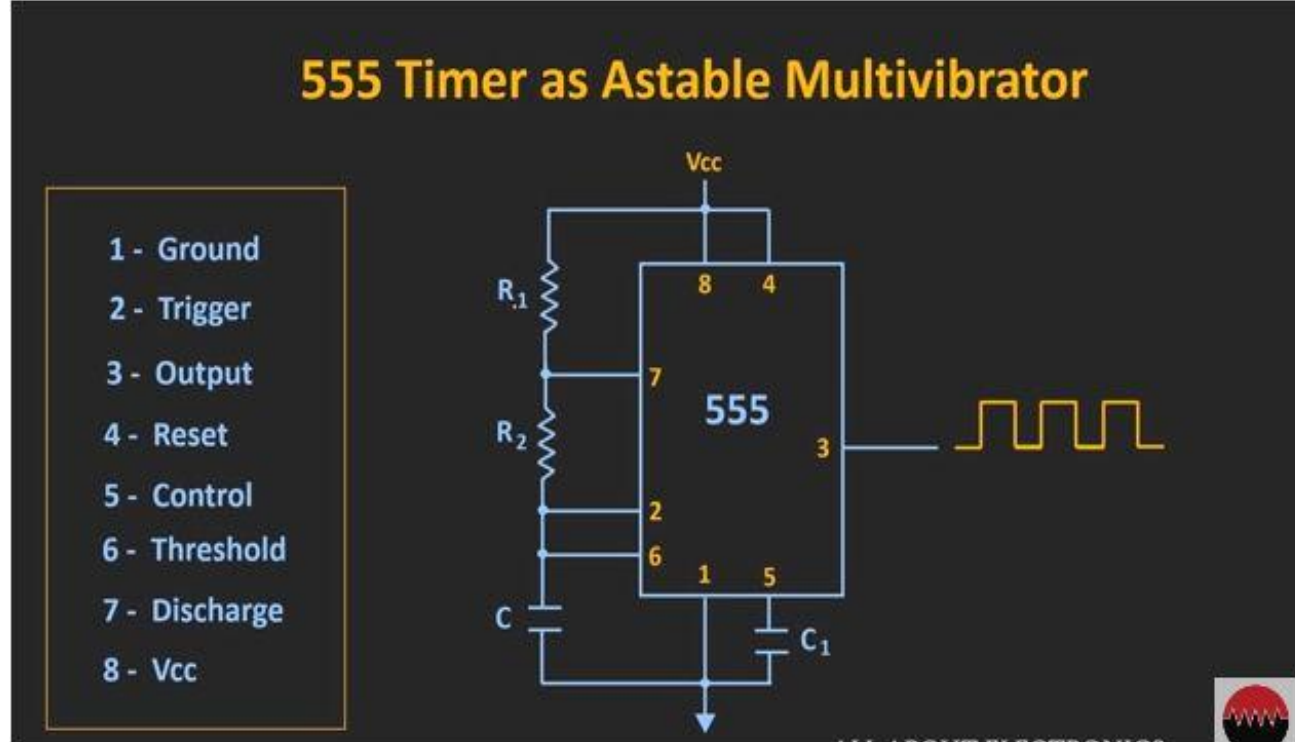Waveform Generation of Astable Multivibrator (555 Timer)




- ✓ Pin 1 is grounded
- ✓ pins 4 and 8 are shorted and then tied to supply +Vcc
- ✓ Output (Vout) is taken from pin 3
- ✓ pin 2 and 6 are shorted and then connected to ground terminal through the capacitor C
- ✓ pin 7 is connected to supply + V_{CC} through a resistor R₁, and between pin 6 and 7, a resistor R₂ is connected
- ✓ At pin 5 a bypass capacitor of 0.01uF is connected (this capacitor is for bypass the noise signals created by resistance divider)

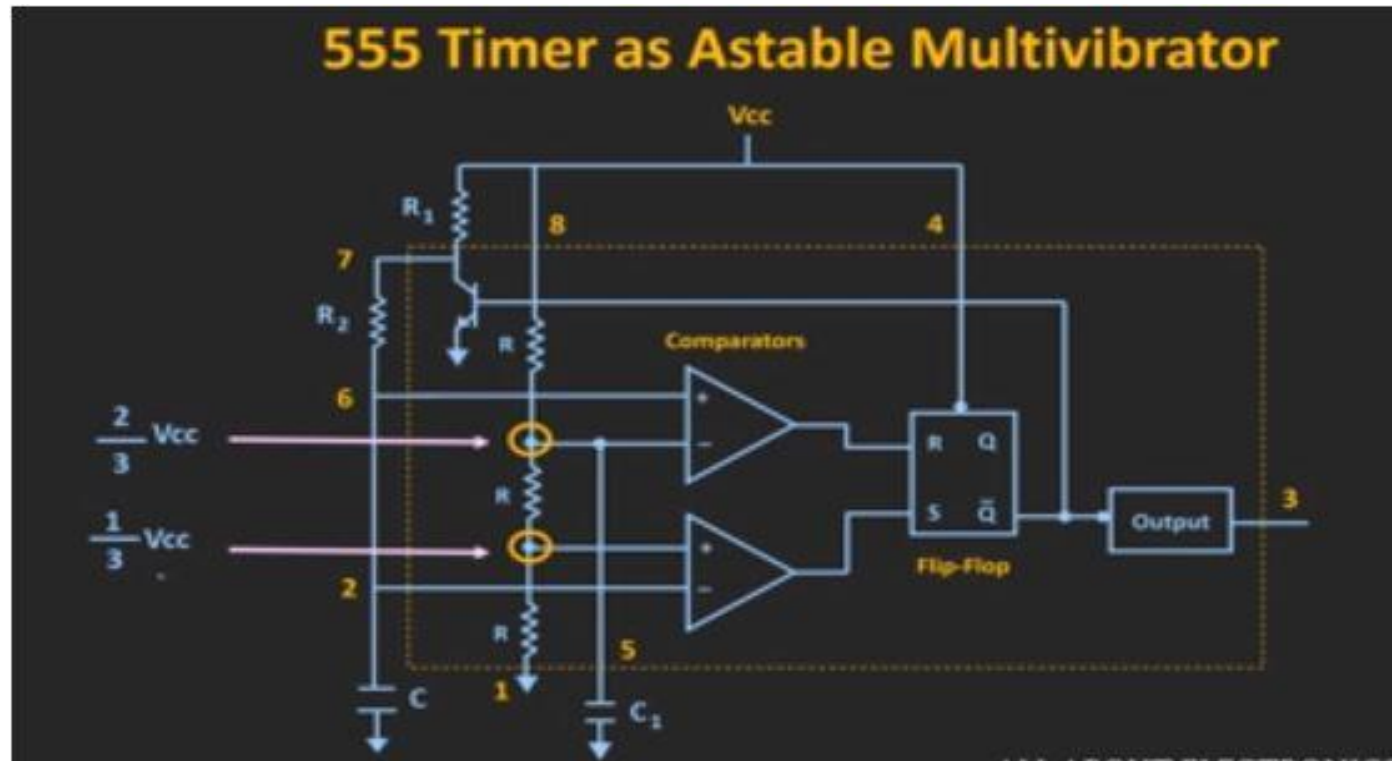
Waveform Generation of Astable Multivibrator (555 Timer)



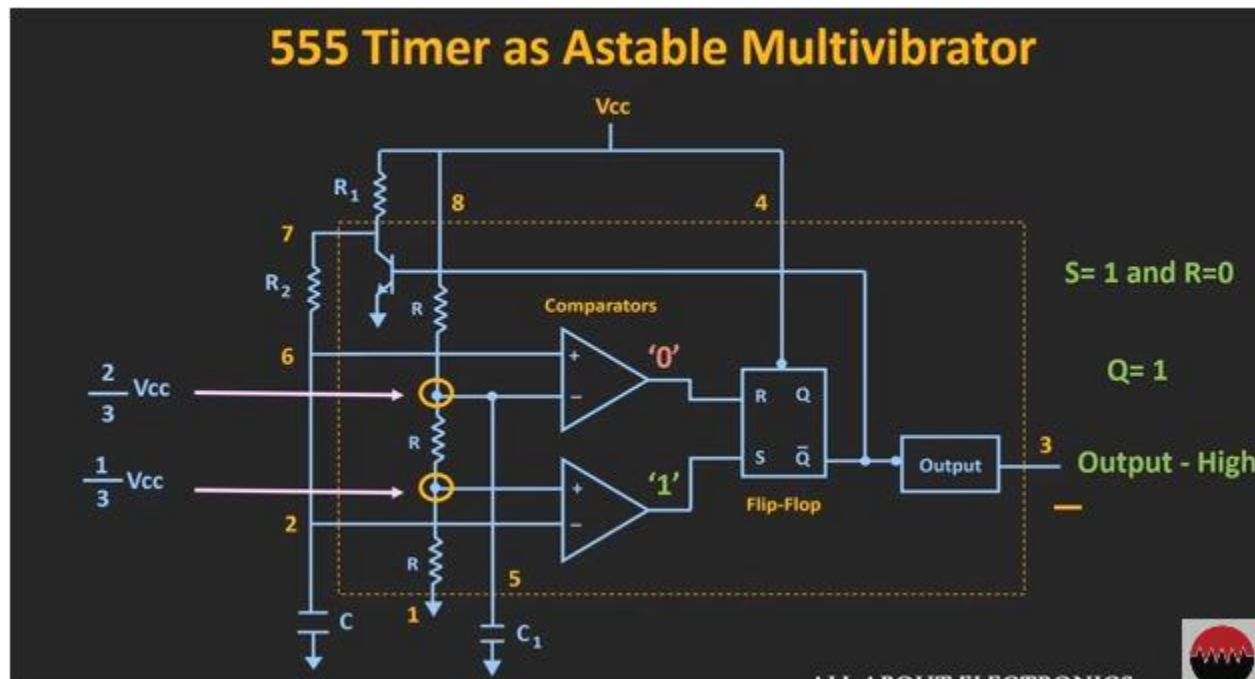
Waveform Generation of Astable Multivibrator (555 Timer)



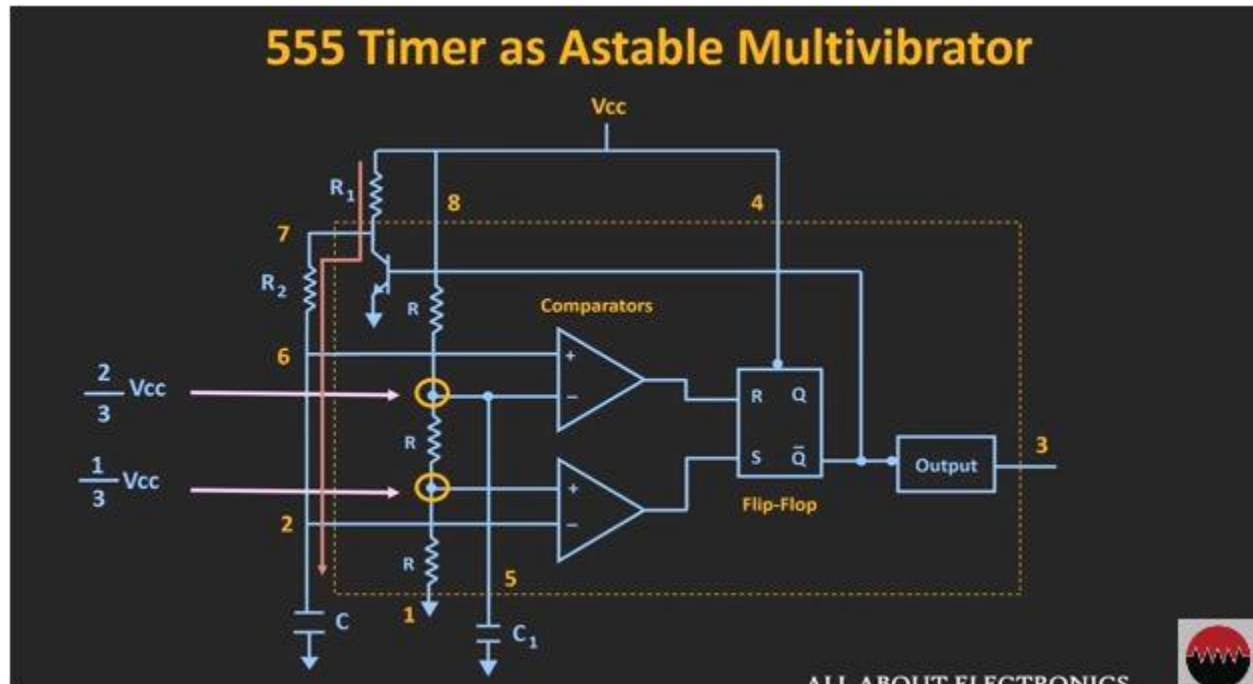
Waveform Generation of Astable Multivibrator (555 Timer)



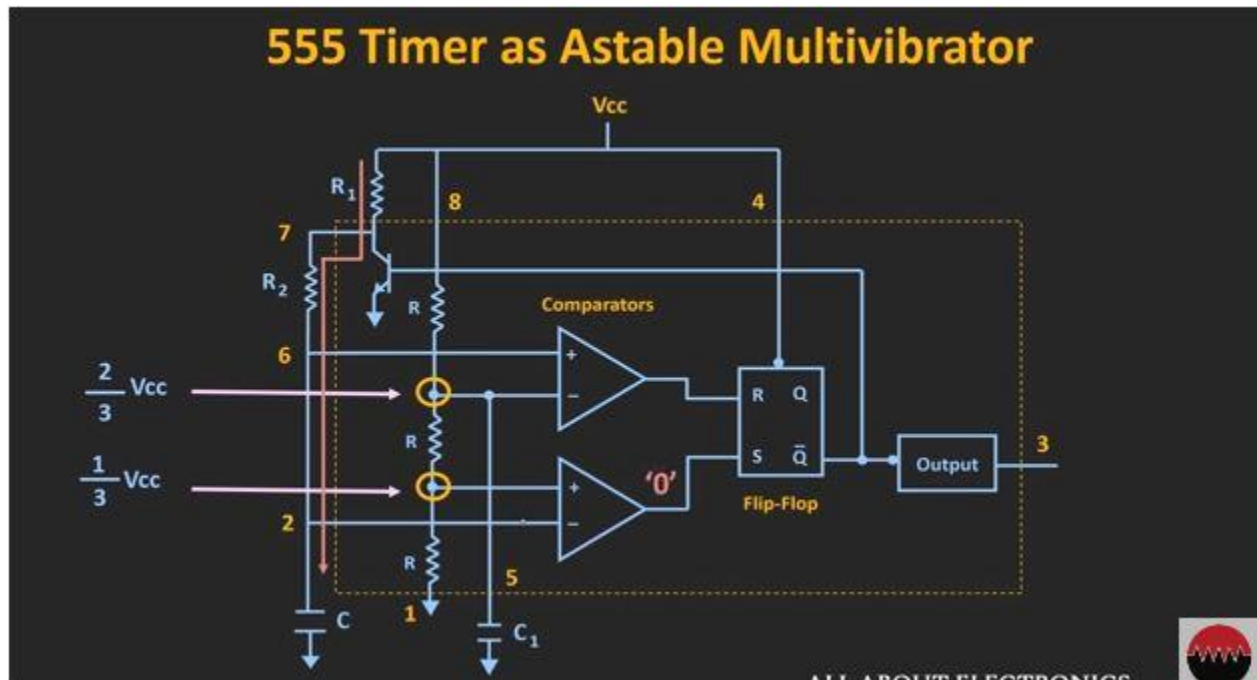
Waveform Generation of Astable Multivibrator (555 Timer)



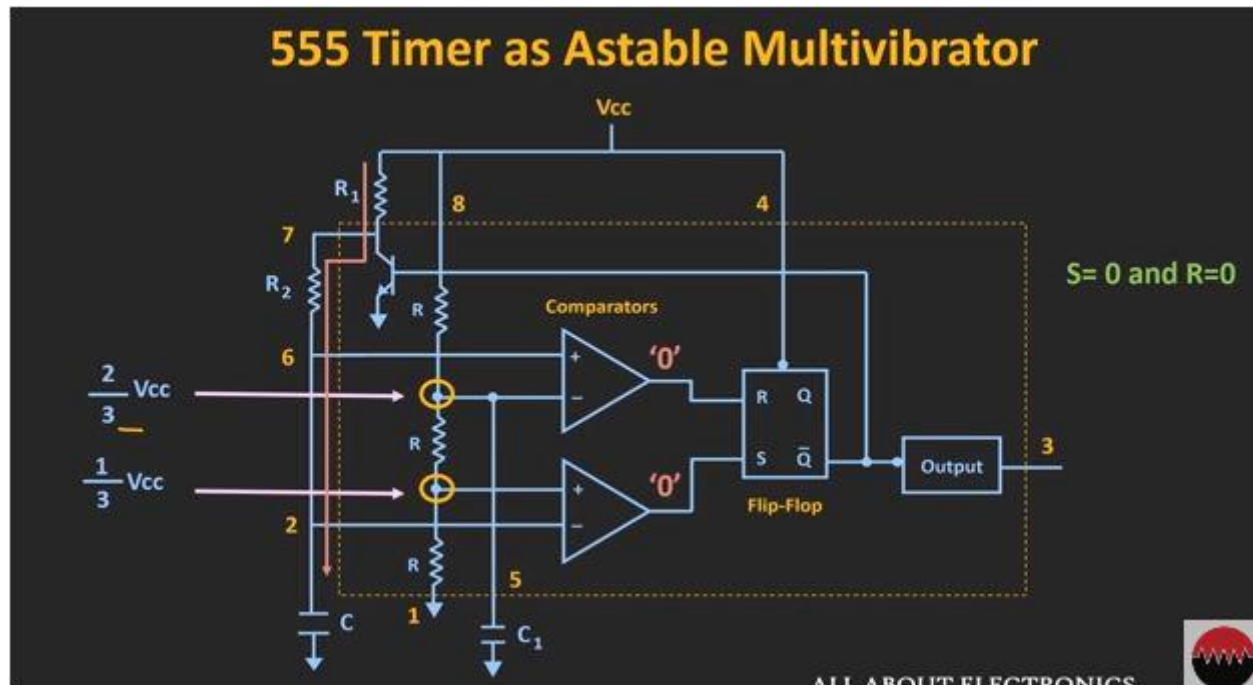
Waveform Generation of Astable Multivibrator (555 Timer)



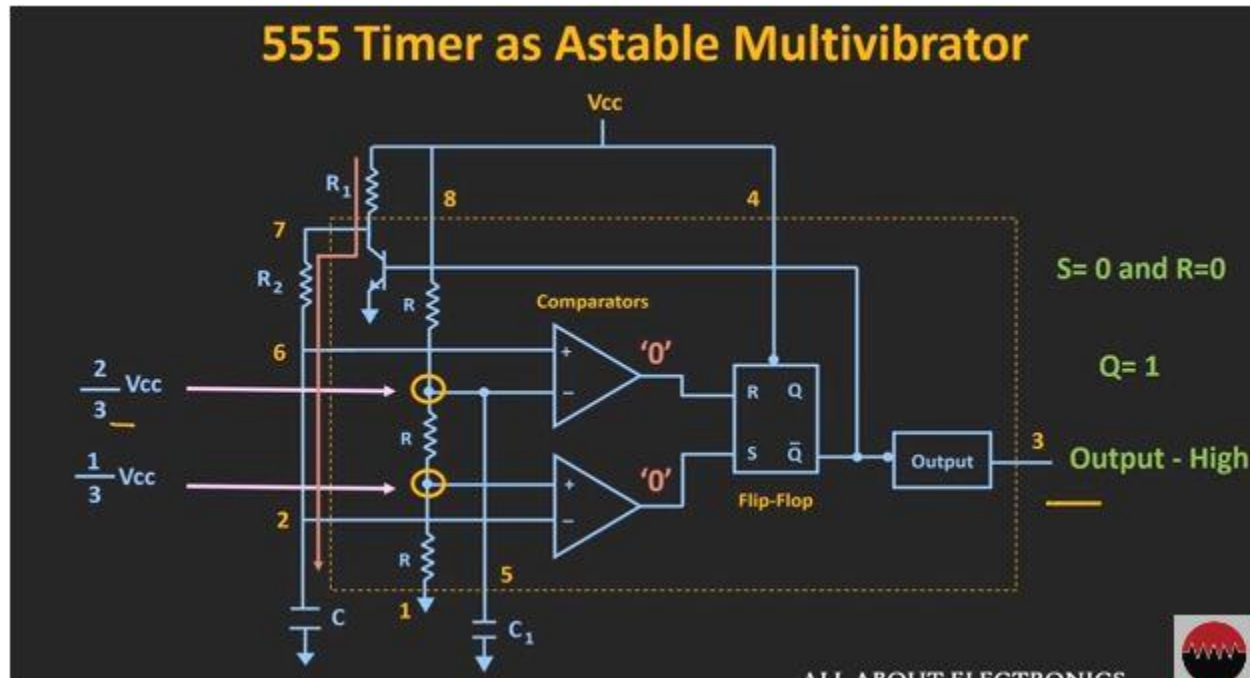
Waveform Generation of Astable Multivibrator (555 Timer)



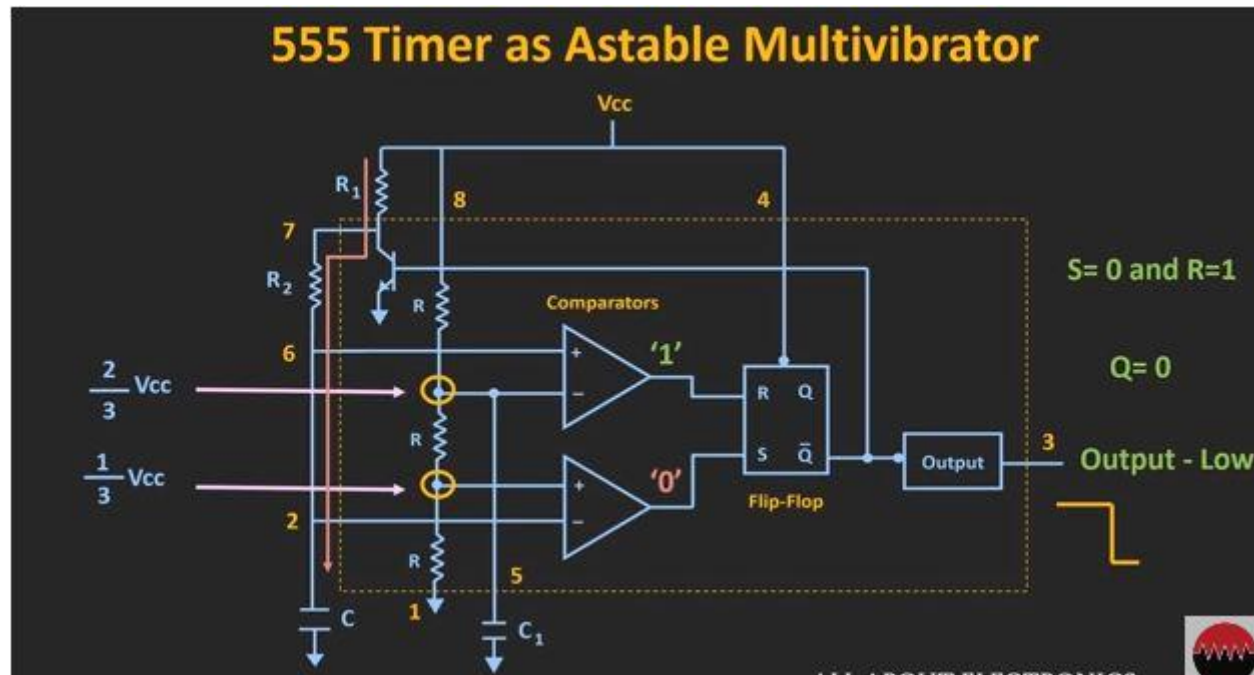
Waveform Generation of Astable Multivibrator (555 Timer)



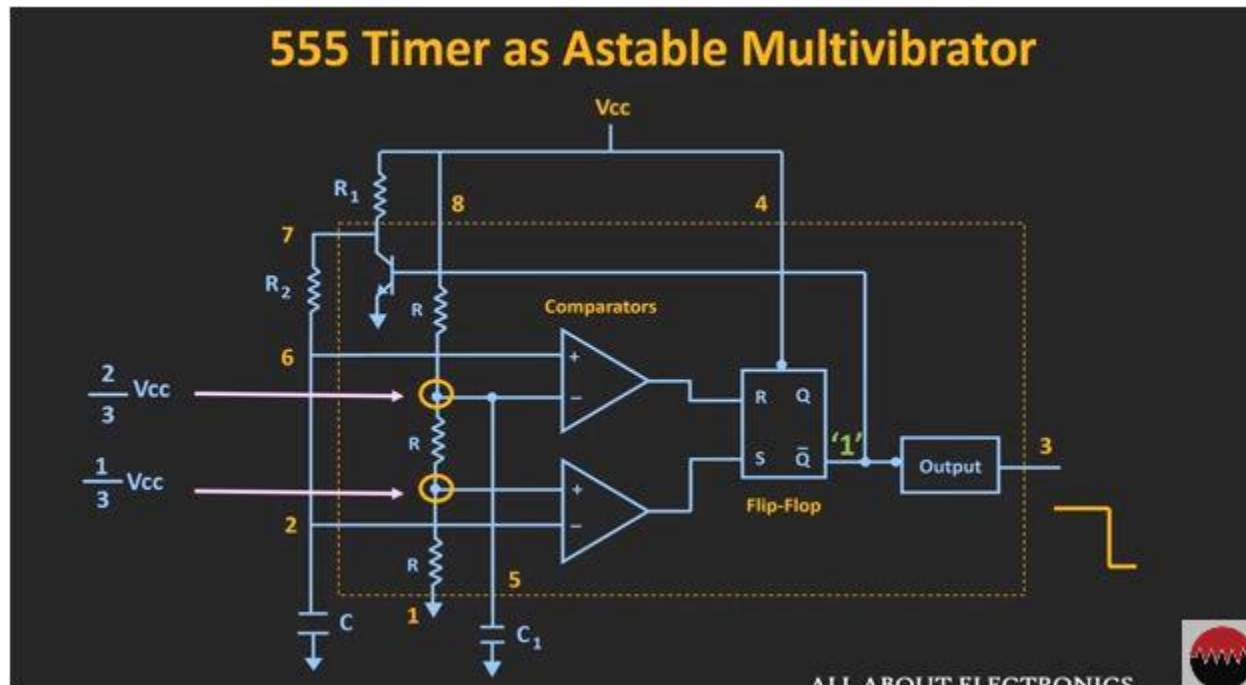
Waveform Generation of Astable Multivibrator (555 Timer)



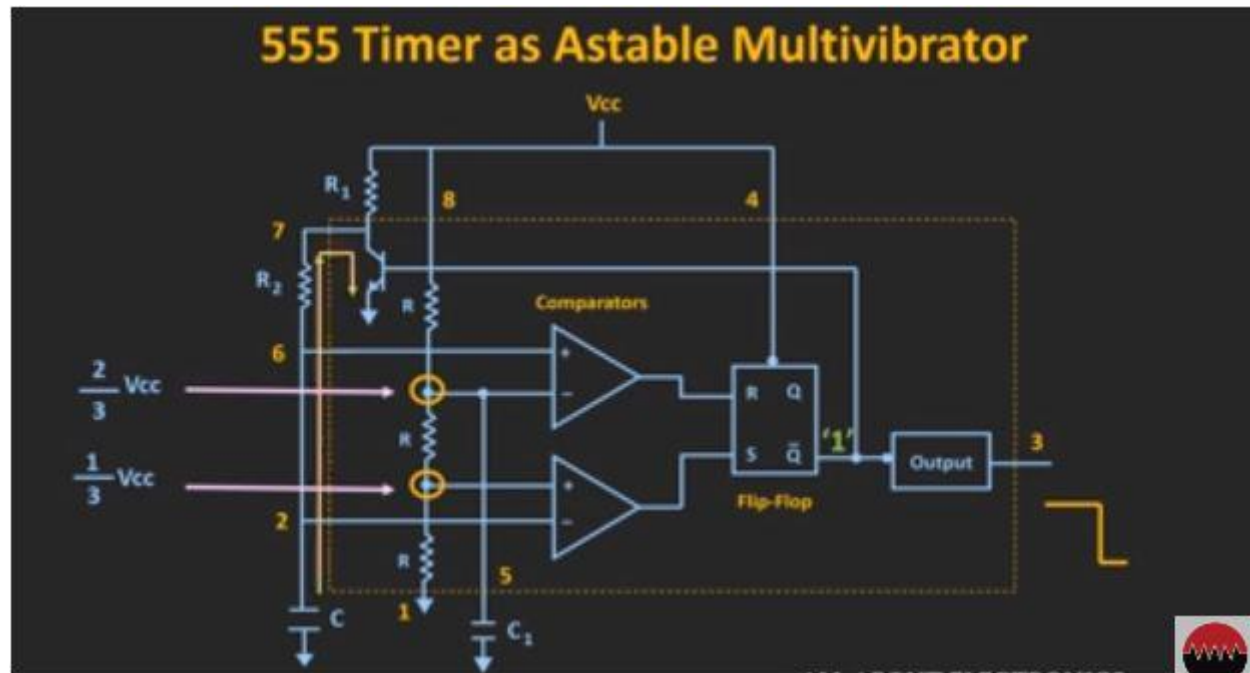
Waveform Generation of Astable Multivibrator (555 Timer)



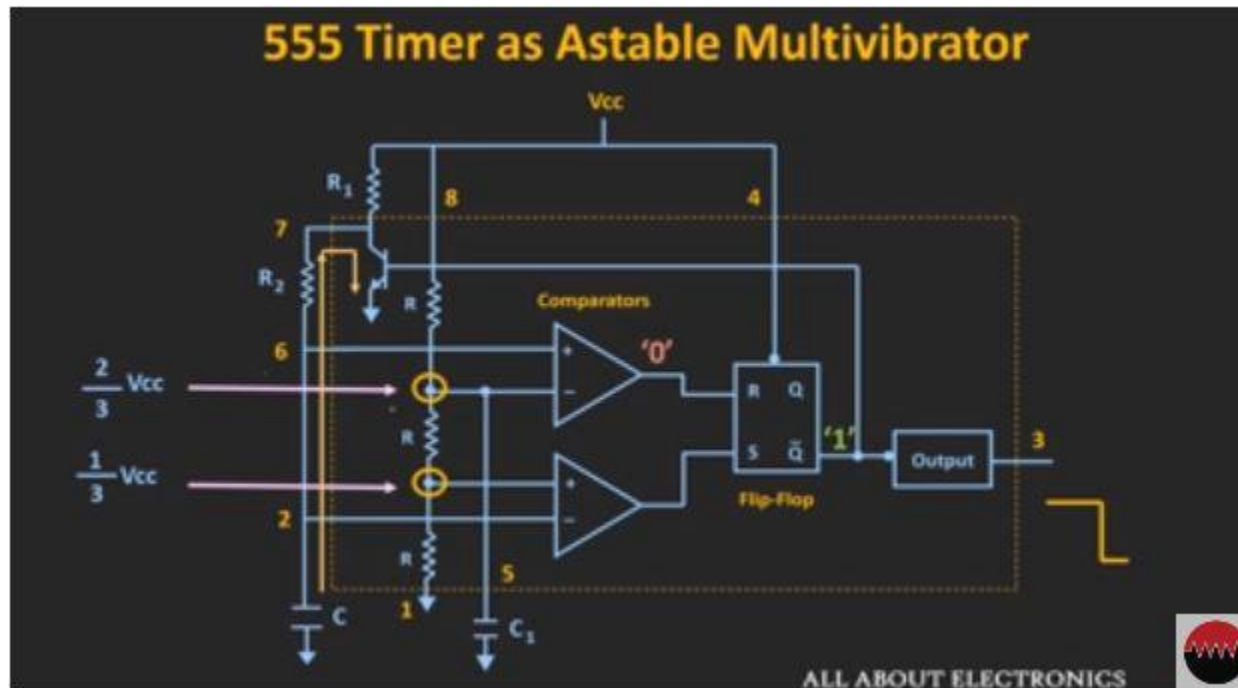
Waveform Generation of Astable Multivibrator (555 Timer)



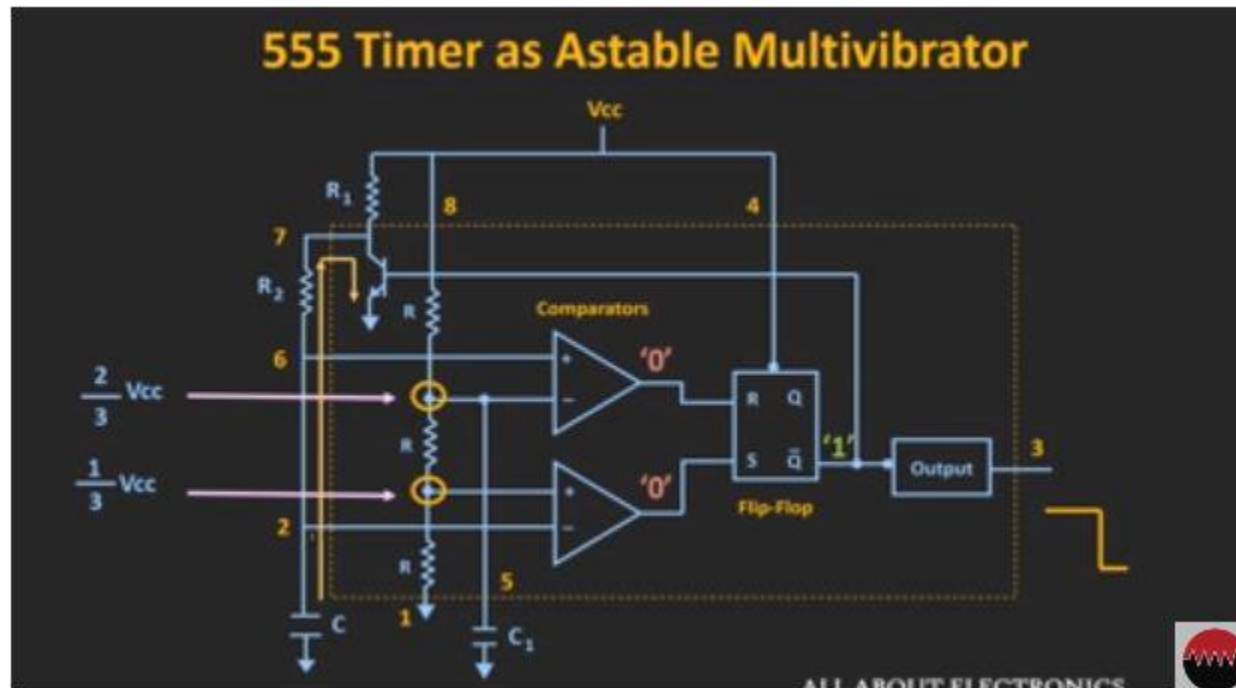
Waveform Generation of Astable Multivibrator (555 Timer)



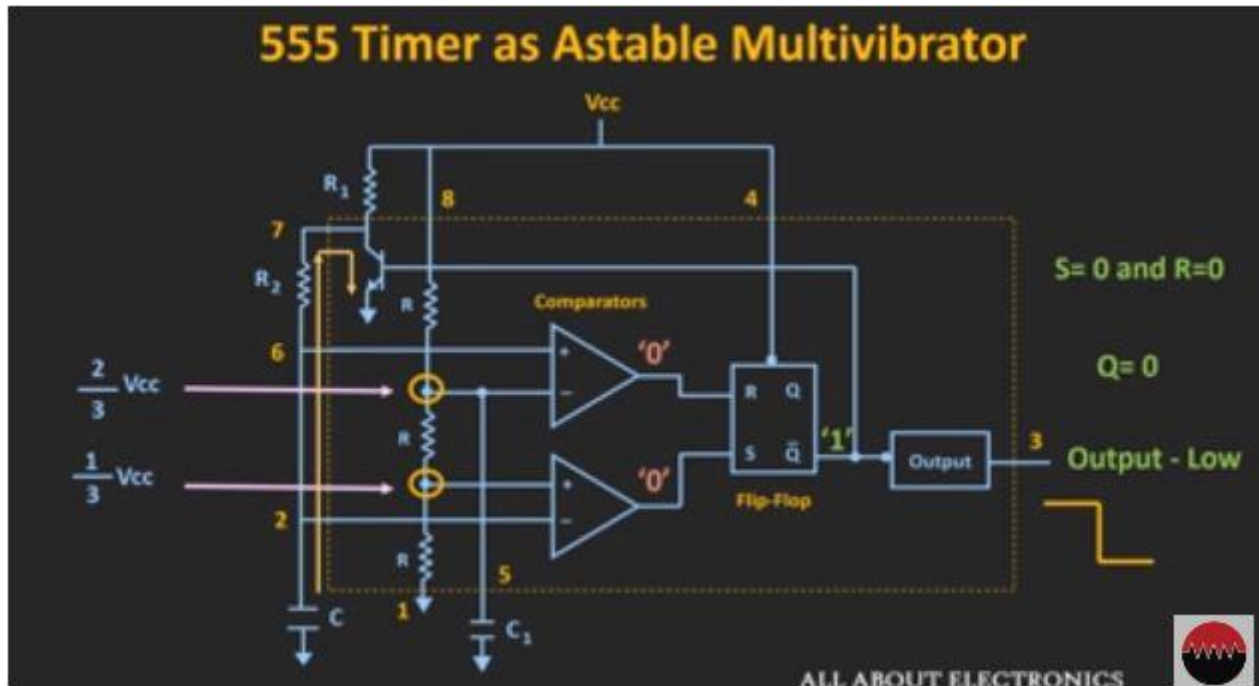
Waveform Generation of Astable Multivibrator (555 Timer)



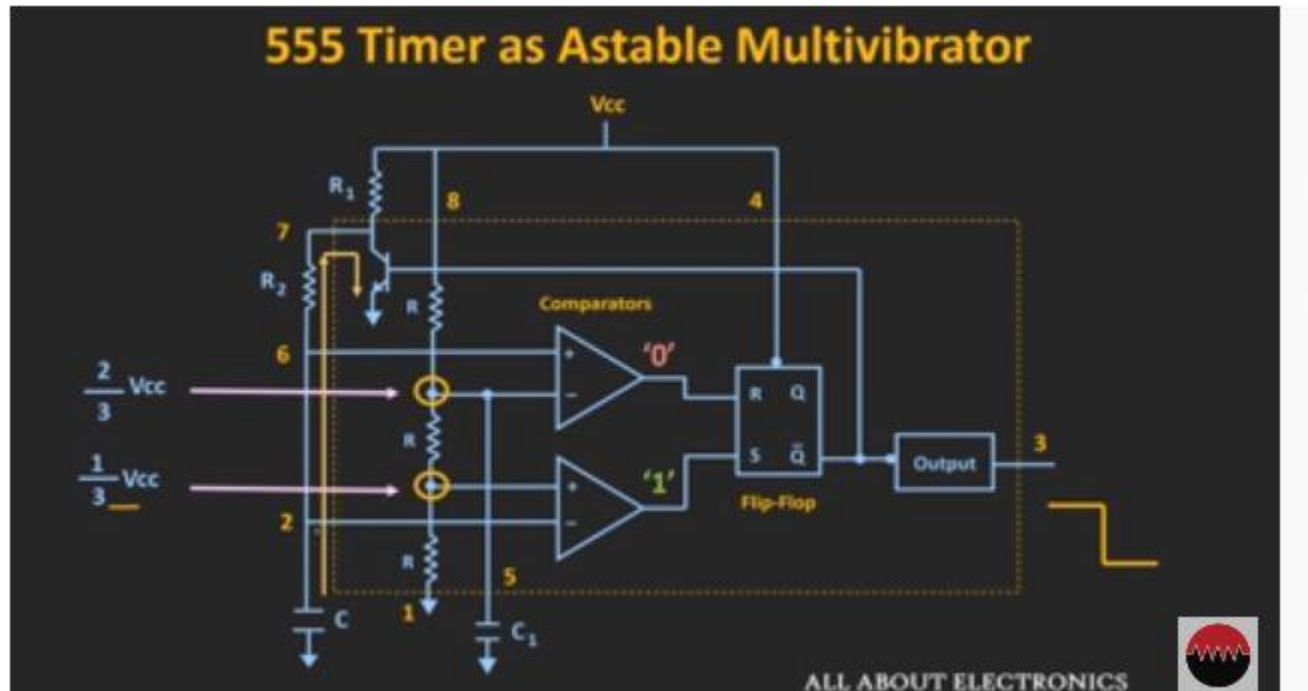
Waveform Generation of Astable Multivibrator (555 Timer)



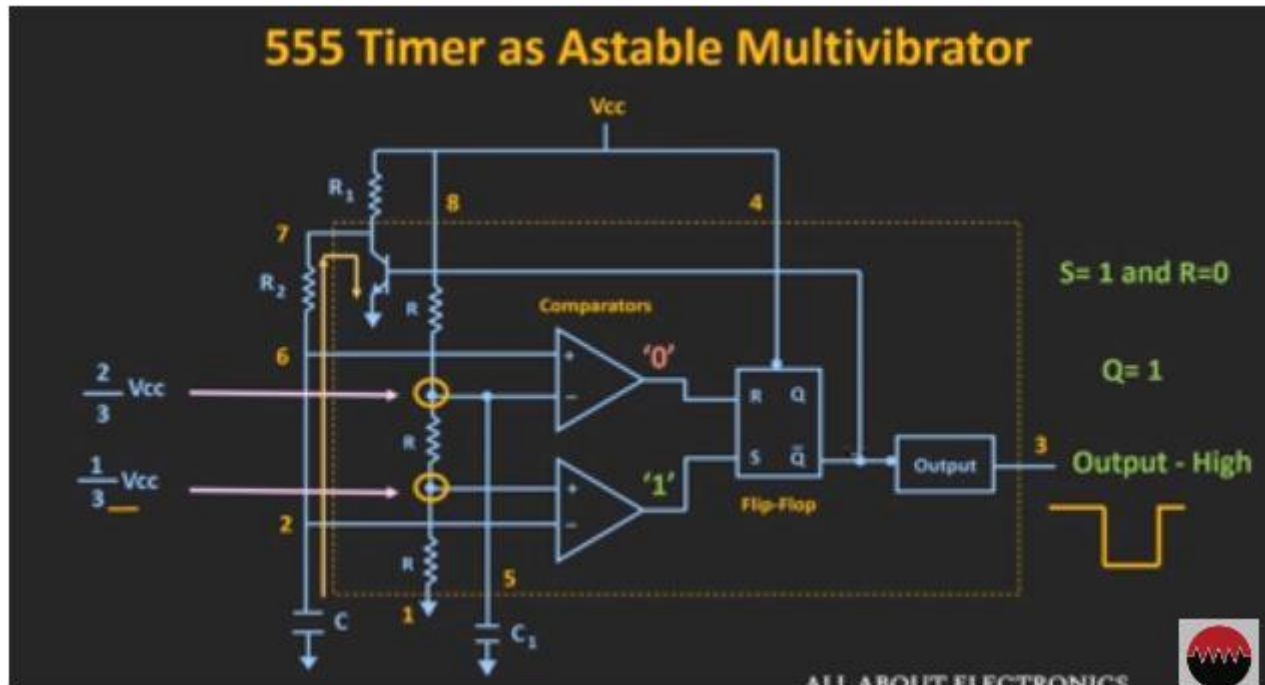
Waveform Generation of Astable Multivibrator (555 Timer)



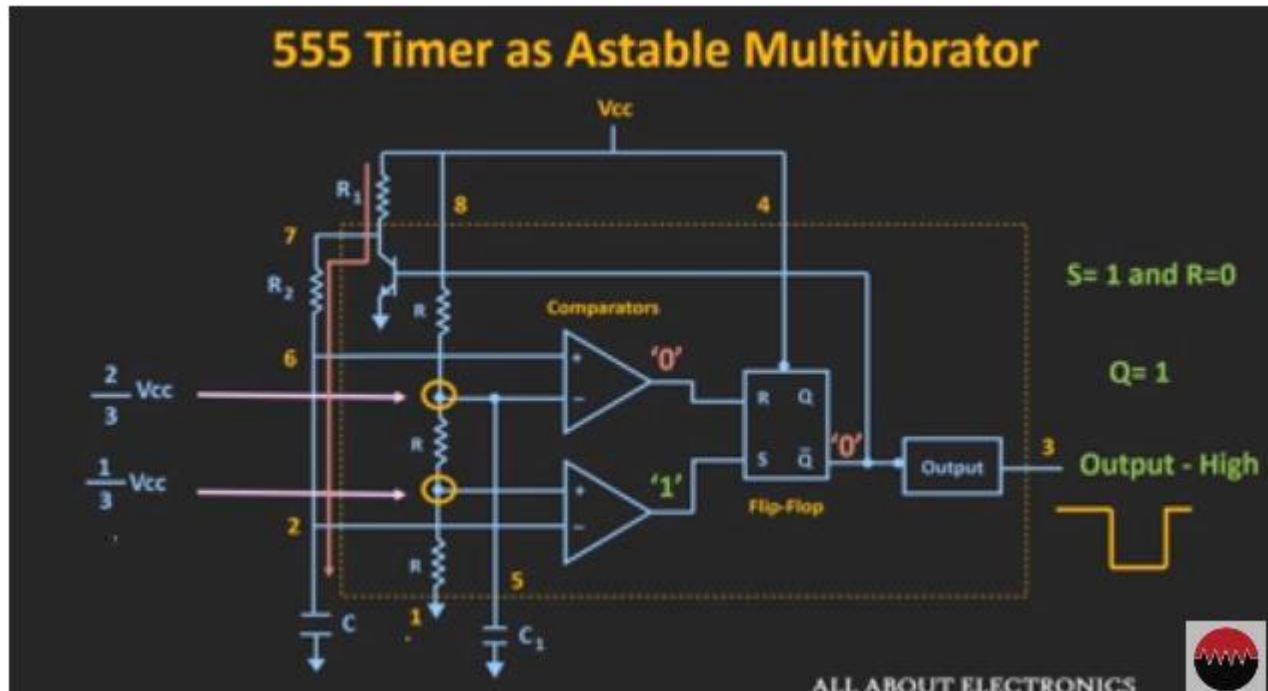
Waveform Generation of Astable Multivibrator (555 Timer)



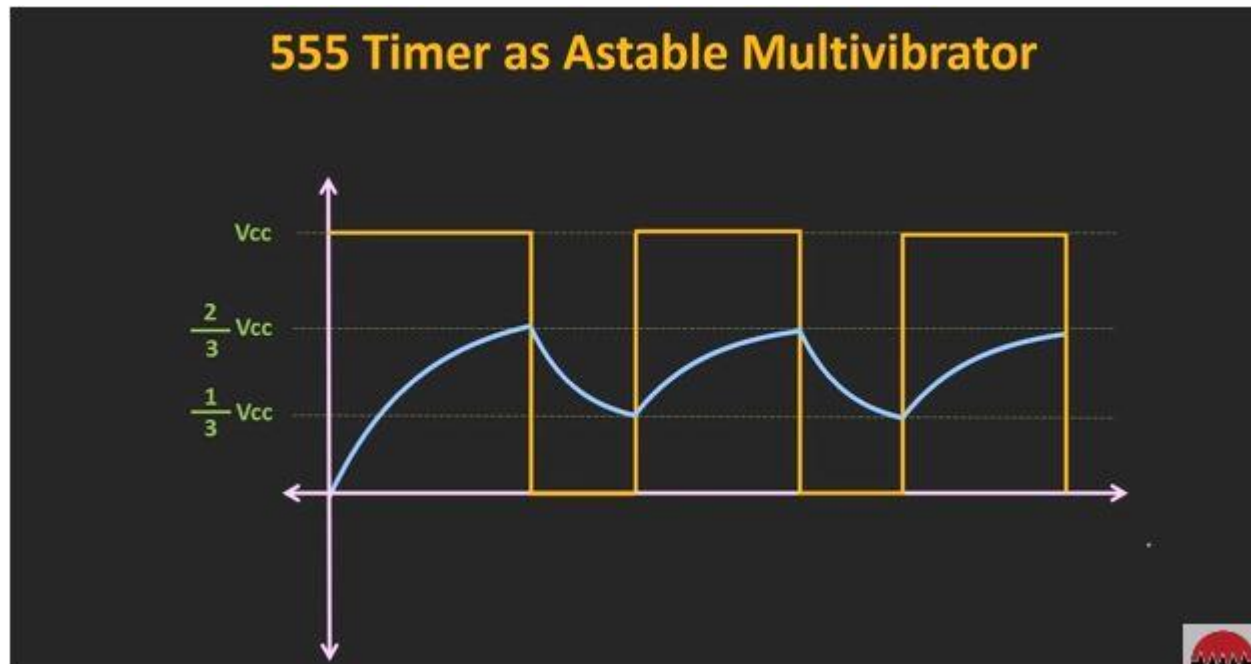Waveform Generation of Astable Multivibrator (555 Timer)



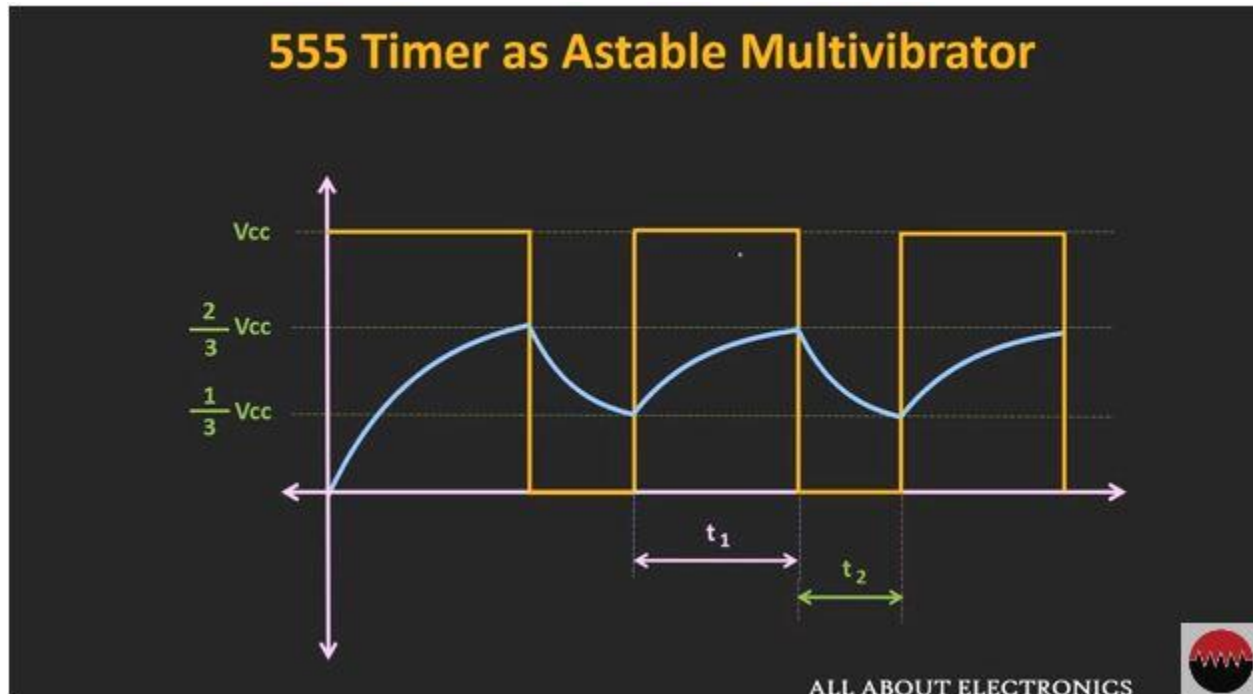
Waveform Generation of Astable Multivibrator (555 Timer)



Waveform Generation of Astable Multivibrator (555 Timer)



555 Timer as Astable Multivibrator

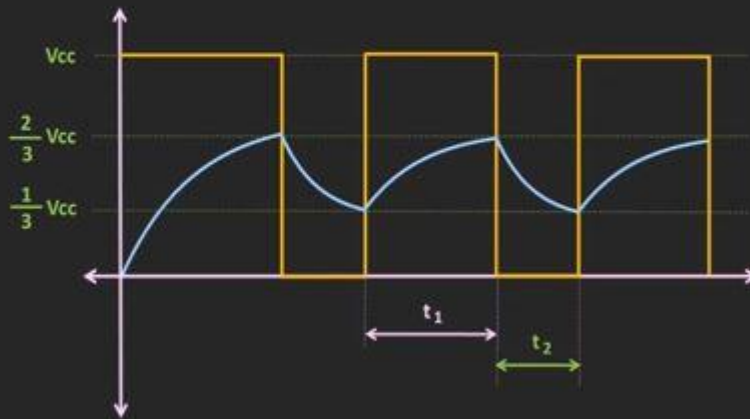


$$t_1 = 0.693 (R_1 + R_2) C$$

$$t_2 = 0.693 R_2 C$$

$$T = t_1 + t_2 = 0.693 (R_1 + 2R_2) C$$

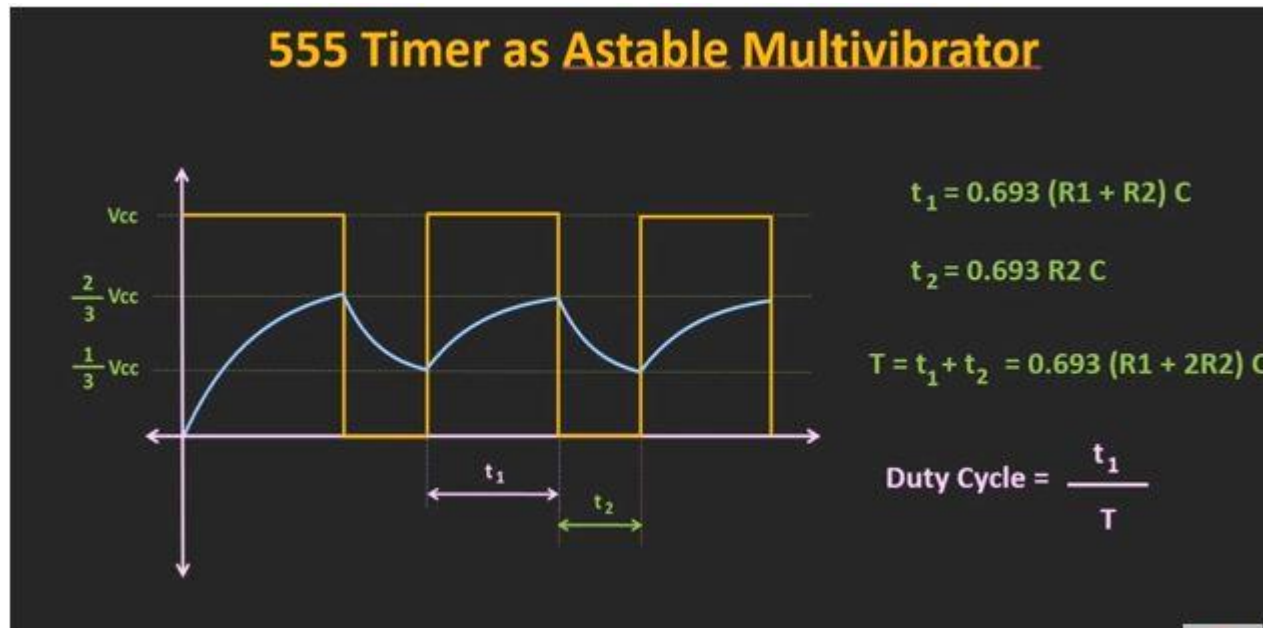
Waveform Generation of Astable Multivibrator (555 Timer)



Waveform Generation of Astable Multivibrator (555 Timer)



555 Timer as Astable Multivibrator

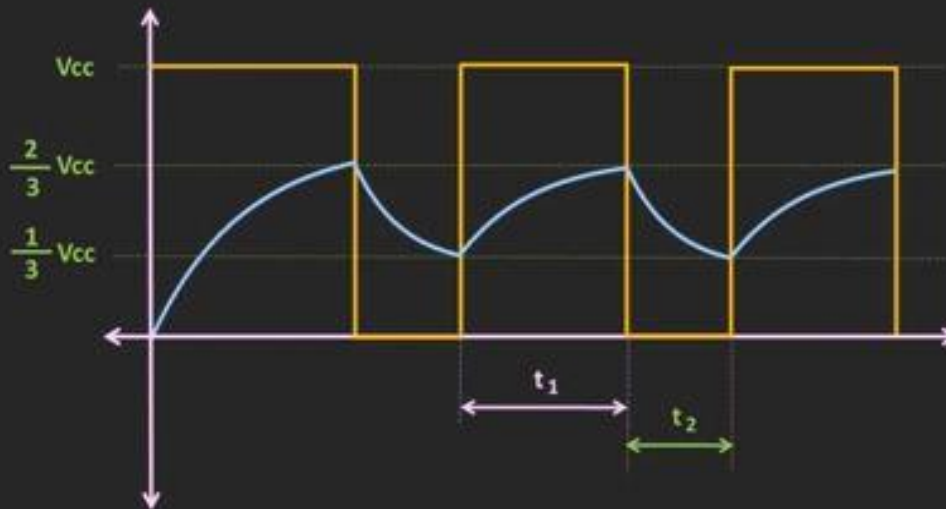

$$t_1 = 0.693 (R_1 + R_2) C$$

$$t_2 = 0.693 R_2 C$$

$$T = t_1 + t_2 = 0.693 (R_1 + 2R_2) C$$

$$\text{Duty Cycle} = \frac{t_1}{T}$$

$$\text{Duty Cycle} = \frac{R_1 + R_2}{R_1 + 2R_2}$$



Numerical Based on Astable Multivibrator (555 Timer)

Q: 1. An **Astable 555 multivibrator** is constructed using the following components, $R_1 = 1\text{k}\Omega$, $R_2 = 2\text{k}\Omega$ and capacitor $C = 10\mu\text{F}$. Calculate the output frequency from the 555 multivibrator.

Solution: T_1 – capacitor charge “ON” time is calculated as:

$$T_1 = 0.693 (R_1 + R_2) \cdot C$$

$$T_1 = 0.693 (1 \times 10^3 + 2 \times 10^3) \cdot 10 \times 10^{-6}$$

$$T_1 = 0.693 (3 \times 10^3) \cdot 10 \times 10^{-6}$$

$$T_1 = 0.021 \text{ s}$$

T_2 – capacitor discharge “OFF” time is calculated as:

$$T_2 = 0.693 (R_2) \cdot C$$

$$T_2 = 0.693 (2000) \cdot 10 \times 10^{-6}$$

$$T_2 = 0.014 \text{ s}$$

Total periodic time (T) is therefore calculated as:

$$T = T_1 + T_2 = 0.021 + 0.014 = 0.035$$

The output frequency, f is therefore given as:

$$f = \frac{1}{T} = \frac{1}{0.035} = 28.57 \text{ Hz}$$

Numerical Based on Astable Multivibrator (555 Timer)

Q: 2. An **Astable 555 multivibrator** is constructed using the following components, $R_1 = 1\text{k}\Omega$, $R_2 = 2\text{k}\Omega$ and capacitor $C = 10\text{ }\mu\text{F}$. Calculate the duty cycle of the output waveform.

Solution:

T_1 – capacitor charge “ON” time is calculated as:

$$T_1 = 0.693 (R_1 + R_2) \cdot C$$

$$T_1 = 0.693 (1 \times 10^3 + 2 \times 10^3) \cdot 10 \times 10^{-6}$$

$$T_1 = 0.693 (3 \times 10^3) \cdot 10 \times 10^{-6}$$

$$T_1 = 0.021\text{ s}$$

T_2 – capacitor discharge “OFF” time is calculated as:

$$T_2 = 0.693 (R_2) \cdot C$$

$$T_2 = 0.693 (2000) \cdot 10 \times 10^{-6}$$

$$T_2 = 0.014\text{ s}$$

Total periodic time (T) is therefore calculated as:

$$T = T_1 + T_2 = 0.021 + 0.014 = 0.035$$

$$\text{Duty Cycle} = \frac{T_1}{T} = \frac{0.021}{0.035} = 0.6 \text{ or } 60\%$$



Thanks